



# Engineering Assignment Coversheet

Student Number(s)

813927

855983

753148

Group Code (if applicable):

Please note that you:

- Must keep a full copy of your submission for this assignment
- Must staple this assignment
- Must NOT use binders or plastic folders except for large assignments

<b>Assignment Title:</b>	VNA Calibration and Measurement
<b>Subject Number:</b>	ELEN90062
<b>Subject Name:</b>	High Speed Electronics
<b>Student Name:</b>	Rui Yuan, Huawang Liu, Haotian Xia
<b>Lecturer/Tutor:</b>	
<b>Due Date:</b>	08/09/2018

## For Late Assignments Only

Has an extension been granted? Yes / No (circle)

A per-day late penalty may apply if you submit this assignment after the due date/extension. Please check with your Department/coordinator for further information.

## Plagiarism

Plagiarism is the act of representing as one's own original work the creative works of another, without appropriate acknowledgment of the author or source.

## Collusion

Collusion is the presentation by a student of an assignment as his or her own which is in fact the result in whole or in part of unauthorised collaboration with another person or persons. Collusion involves the cooperation of two or more students in plagiarism or other forms of academic misconduct.

Both collusion and plagiarism can occur in group work. For examples of plagiarism, collusion and academic misconduct in group work please see the University's policy on Academic Honesty and Plagiarism:

<http://academichonesty.unimelb.edu.au/>

Plagiarism and collusion constitute cheating. Disciplinary action will be taken against students who engage in plagiarism and collusion as outlined in University policy. Proven involvement in plagiarism or collusion may be recorded on my academic file in accordance with Statute 13.1.18.

## STUDENT DECLARATION

Please sign below to indicate that you understand the following statements:

I declare that:

- This assignment is my own original work, except where I have appropriately cited the original source.
- This assignment has not previously been submitted for assessment in this or any other subject.

For the purposes of assessment, I give the assessor of this assignment the permission to:

- Reproduce this assignment and provide a copy to another member of staff; and
- Take steps to authenticate the assignment, including communicating a copy of this assignment to a checking service (which may retain a copy of the assignment on its database for future plagiarism checking).

Student signature

*Haotian Xia*  
*Rui Yuan Huawang*

08/09/2018

Date



University of Melbourne  
ELEN90062 High Speed Electronics  
WORKSHOP

# WORKSHOP 3 REPORT

---

Rui YUAN  
813927  
Huawang Liu  
855983  
Haotian Xia  
753148

September 5, 2018

---

# 1 Task 1

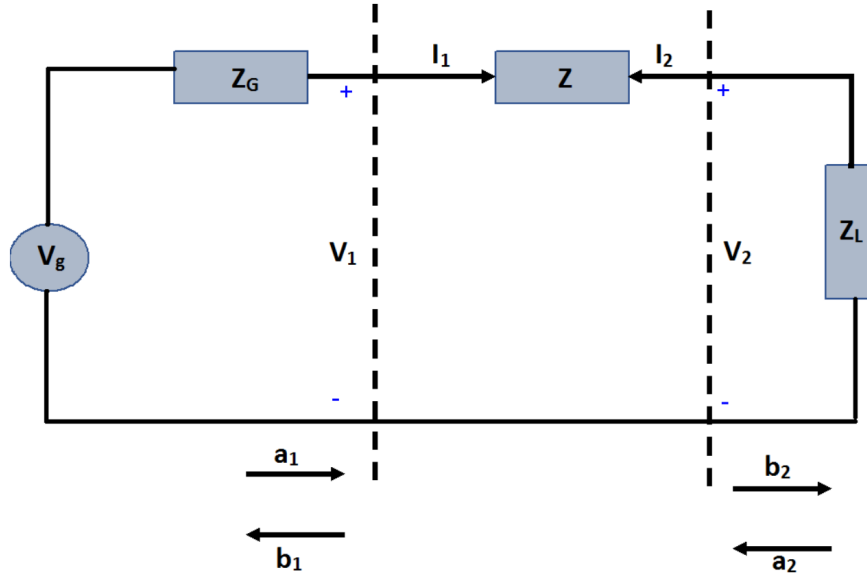


Figure 1: Two port network

Based on the two equations in guidebook, since  $Z_G = Z_0$ ,  $Z = 0$ , then  $V_1 = V_2$ , by definition, since no wave coming into port 2,  $a_2 = 0$ . From the figure, we have:

$$a_1 = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}} \quad (1)$$

$$b_1 = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}} \quad (2)$$

$$\begin{aligned} S_{11} &= \frac{b_1}{a_1} \Big|_{a_2=0} \\ &= \frac{V_1 - I_1 Z_0}{V_1 + I_1 Z_0} \\ &= \frac{\frac{V_1}{I_1} - Z_0}{\frac{V_1}{I_1} + Z_0} \\ &= \frac{Z + Z_L - Z_0}{Z + Z_L + Z_0} \end{aligned} \quad (3)$$

Since we are given  $Z = 0$ , we have:  $S_{11} = \frac{Z_L - Z_0}{Z_L + Z_0}$

## 2 Task 2

Under this circumstance, from figure 1, we have:

$$a_2 = \frac{V_2 + I_2 Z_0}{2\sqrt{Z_0}} = \frac{V_2 + I_2 Z_l}{2\sqrt{Z_0}} = 0 \quad (4)$$

$$\begin{aligned} S_{21} &= \frac{b_2}{a_1} \Big|_{a_2=0} \\ &= \frac{V_2 - I_2 Z_0}{V_1 + I_1 Z_0} \\ &= \frac{2V_2}{I_1(Z + Z_L) + I_1 Z_0} \\ &= \frac{2Z_L}{Z + Z_L + Z_0} \\ &= \frac{2Z_0}{Z + 2Z_0} \end{aligned} \quad (5)$$

## 3 Task 3

The smith charts plotted as below:

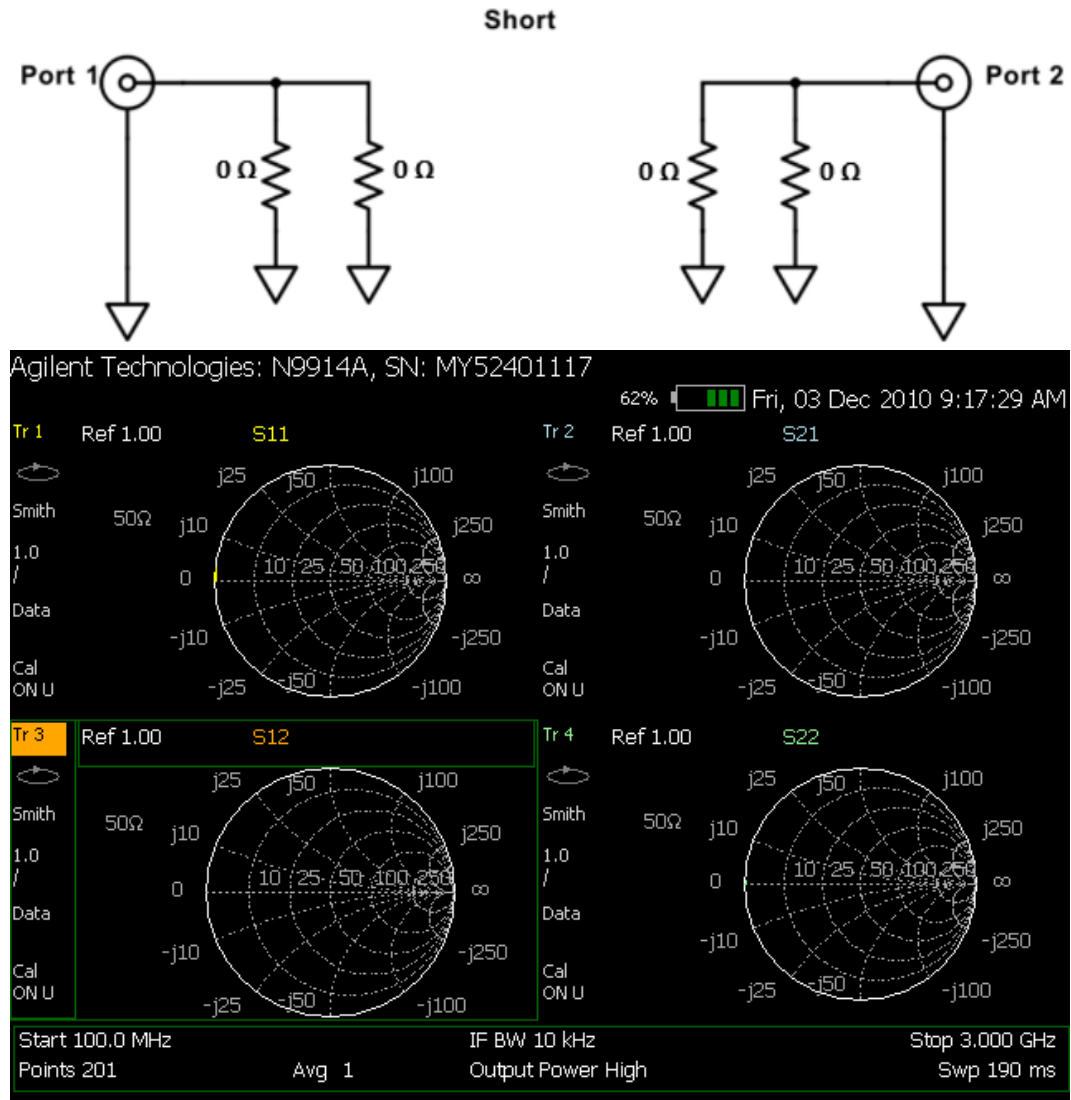


Figure 2: Short circuit SOLT connected

From the figure above, we have calibrated Port extension to make our circuit match.  $Z_L = Z_G = 0\Omega$ ,  $Z = \infty$ . Hence,  $I_1 = I_2 = 0$ ,  $V_1 = 0$ . From equation 1, we have  $a_1 = 0$ , our  $S_{22} = 1$ .  $S_{22}$

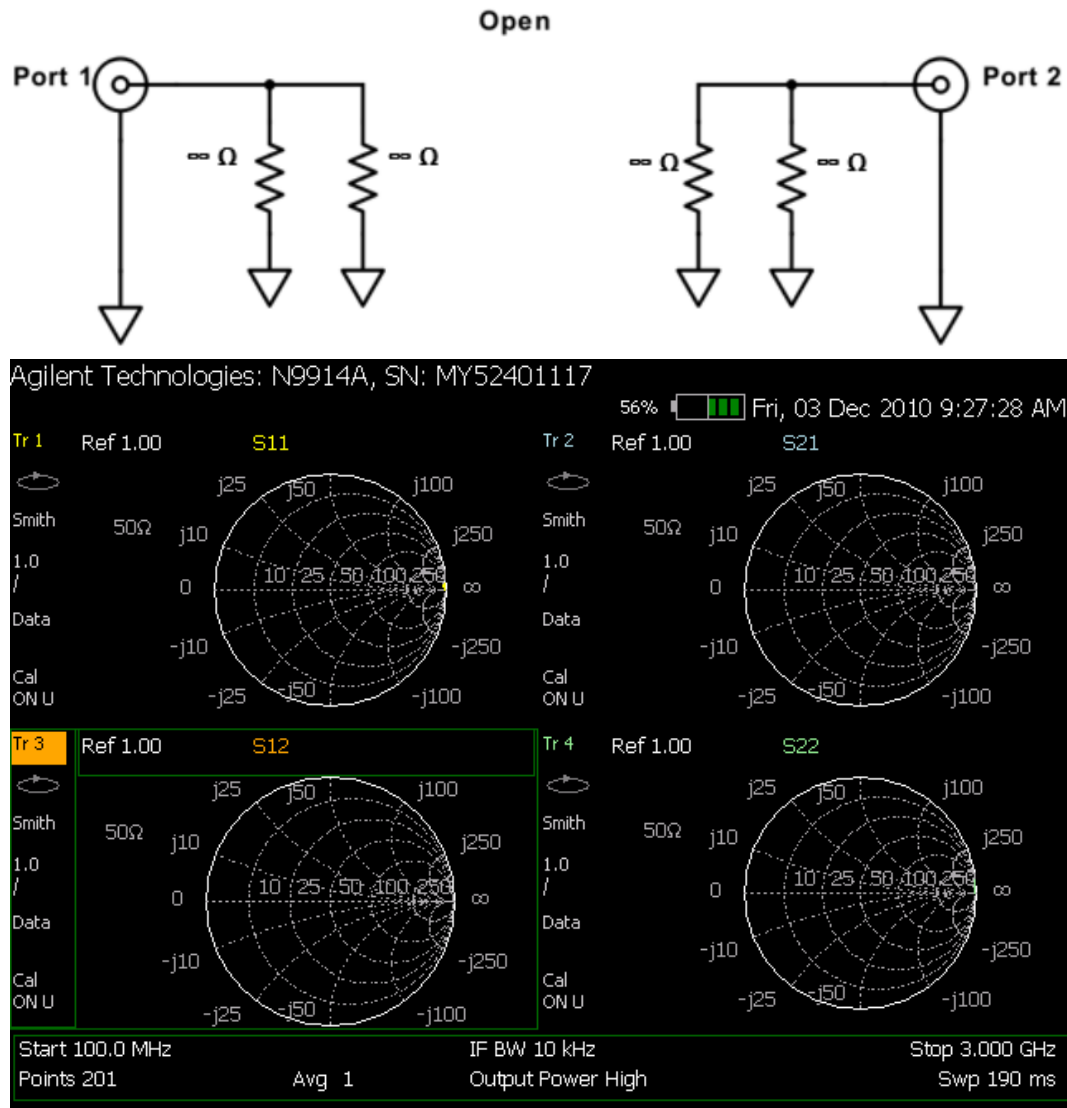


Figure 3: Open circuit SOLT connected

From the figure above, as  $Z = Z_L = Z_G = \infty$ . Hence,  $I_1 = I_2 = 0$ ,  $V_2 = 0$ . from equation (4), our  $S_{11} = \infty$  why  $S_{22}$

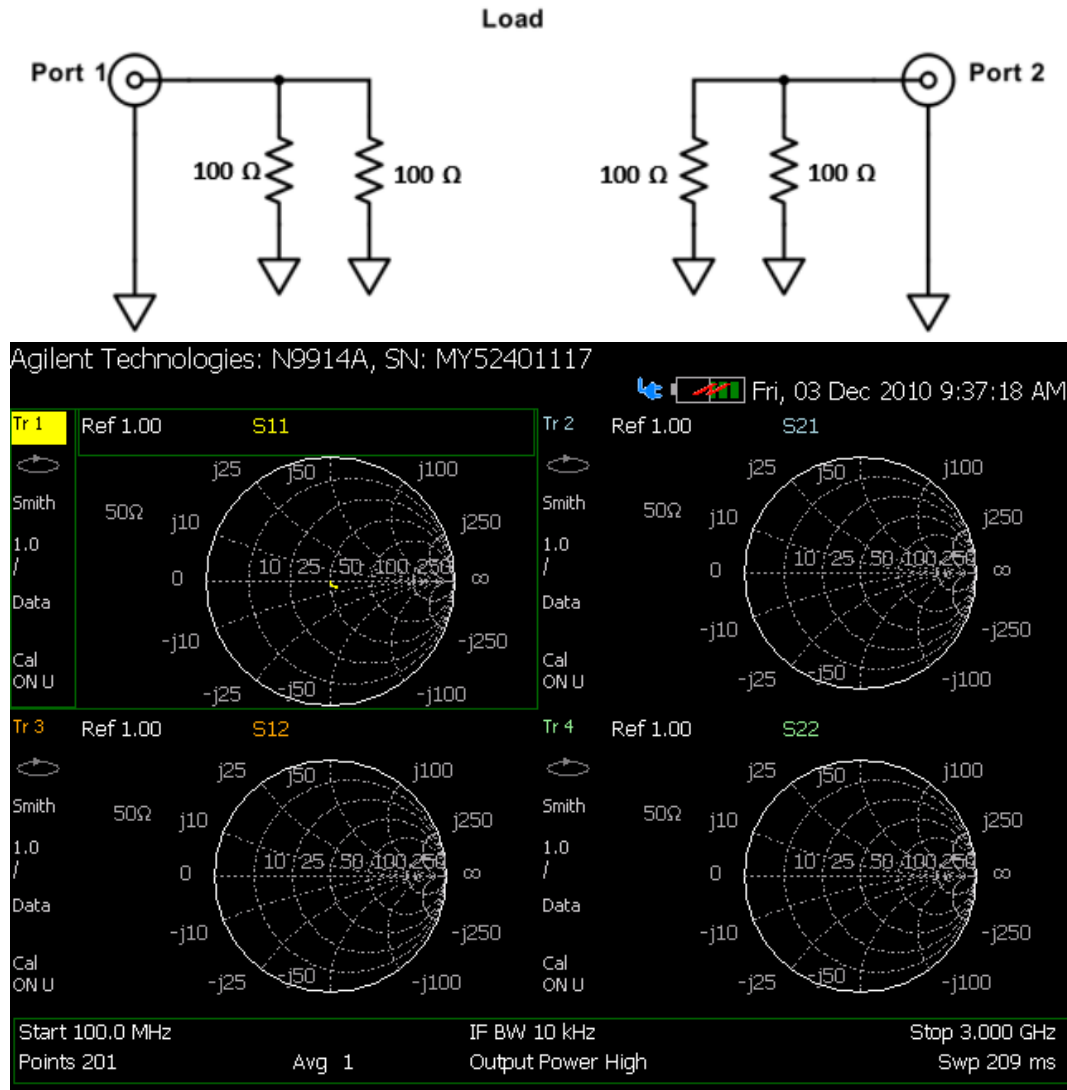


Figure 4: Load circuit SOLT connected

From the figure above, as  $Z_0 = Z_L = Z_G = 50\Omega$ ,  $Z = 0\Omega$ . Hence, from equation (3), our  $S_{11} = 0$ .  $S_{22}$

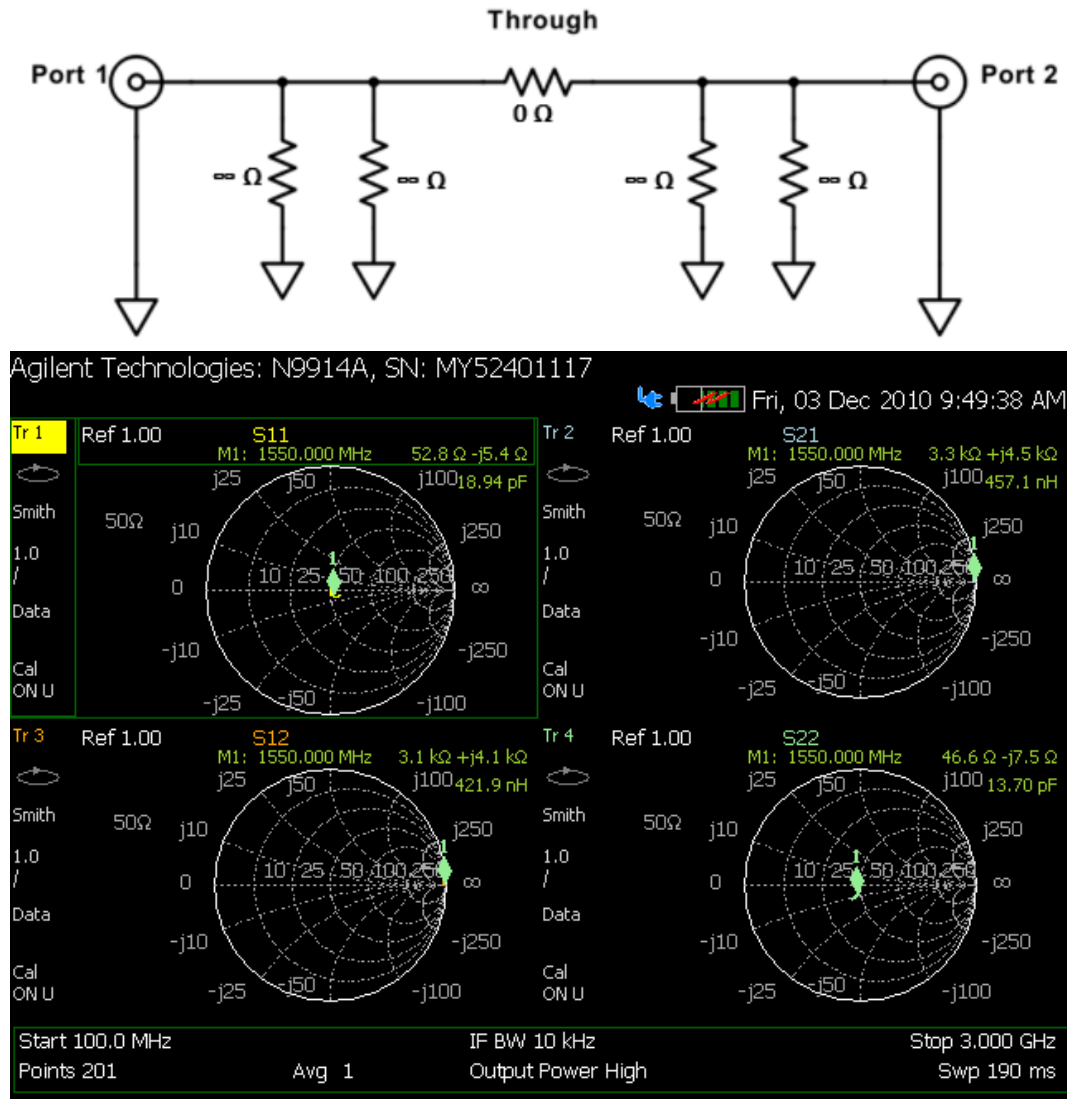


Figure 5: Through circuit SOLT connected

From the figure 5 above,  $Z_G = Z_L = Z_0 = 50\Omega$ ,  $Z = 0\Omega$ , based on equation (3),  $S_{11} = 0$

## 4 Task 4

Open the data file with excel, we have the figure 6, by checking



## 4.1 Shunt1

IS2P	File:	Measurem	S21	S12	S22:			
#	Hz	S	DB	R	50			
1E+08	-0.00155	-19.7431	-80.79	-145.367	-82.8349	45.94263	0.029643	7.732607
1.15E+08	-0.06393	-22.2874	-86.1061	87.81405	-75.2582	-32.3697	0.021865	8.925692
1.29E+08	-0.14092	-24.9997	-71.7224	169.6007	-81.044	143.8072	0.003878	10.03125
1.44E+08	-0.17129	-27.8953	-79.5867	-57.6529	-78.1726	112.8304	-0.00834	11.04866
1.58E+08	-0.14915	-30.7957	-79.0712	80.20201	-75.3253	-83.403	0.016574	12.09898
1.73E+08	-0.09048	-33.6225	-92.6586	-124.22	-77.1235	139.5885	0.030625	13.15535
1.87E+08	-0.04318	-36.1847	-80.4571	110.8596	-80.7933	139.6903	0.0428	14.27817
2.02E+08	-0.07476	-38.4871	-87.5648	-135.034	-78.3288	-68.5177	0.05715	15.56697
2.16E+08	-0.14338	-41.0119	-84.7827	179.5088	-89.1524	67.79482	0.044337	16.69759
2.31E+08	-0.20487	-43.4405	-72.6304	-45.5363	-80.5562	-120.055	0.03487	17.73499
2.45E+08	-0.21509	-46.209	-76.7595	96.67597	-80.7322	-38.9185	0.031068	18.77086
2.6E+08	-0.16701	-48.8092	-86.0454	-76.9514	-77.6622	68.55026	0.052749	19.81303
2.74E+08	-0.11001	-51.3164	-77.7181	-51.9178	-78.7879	175.7009	0.073038	20.94815
2.89E+08	-0.12318	-53.6266	-79.8211	-49.2857	-78.5502	145.8896	0.093835	22.12992
3.03E+08	-0.16318	-55.6441	-68.6995	-128.783	-77.0061	-132.134	0.095951	23.37715
3.18E+08	-0.23166	-57.643	-76.5221	-123.103	-85.883	134.3924	0.079685	24.43528
3.32E+08	-0.27237	-59.9851	-81.1789	93.79252	-70.246	160.7273	0.065101	25.47345
3.47E+08	-0.28491	-62.3539	-81.4632	-167.501	-75.0175	-76.6009	0.076678	26.53218
3.61E+08	-0.22498	-64.6918	-78.301	91.61384	-80.2436	-119.778	0.104399	27.57803
3.76E+08	-0.19423	-66.6771	-80.3931	-74.7146	-89.1061	-78.058	0.12916	28.70275
3.9E+08	-0.20643	-68.5889	-88.4409	179.9353	-85.924	1.12408	0.145411	29.95759
4.05E+08	-0.27135	-70.341	-79.961	104.8055	-78.3824	-161.725	0.148569	31.21896
4.19E+08	-0.32825	-72.0813	-72.606	-72.772	-83.7169	88.90123	0.139017	32.33455
4.34E+08	-0.34964	-74.2057	-85.9524	51.02423	-76.3326	8.911616	0.128271	33.36544
4.48E+08	-0.32756	-76.2046	-81.6856	-169.456	-82.832	-136.499	0.141123	34.40829
4.63E+08	-0.28727	-78.2469	-79.028	35.01264	-78.0834	-114.852	0.165747	35.50906
4.77E+08	-0.27304	-79.8556	-86.1182	128.1715	-75.1437	89.77458	0.187567	36.64943

Figure 6: S2P data for shunt 1

By observation, the first shunt is a capacitor. Based on equation 3:

$$S_{11} = \frac{\frac{1}{j2\pi fc} - Z_0}{\frac{1}{j2\pi fc} + Z_0} \quad Z_0 = 50\Omega \quad (6)$$

$$c = \frac{1 - S_{11}}{100j\pi f(1 + S_{11})} \quad (7)$$

We cannot get the answer with only the abs of  $S_{11}$ , the abs should always be 1 no matter what c value it is!!. Magnitude-phase.

## 4.2 Shunt2

Since this load is a pure resistor:

$$S_{11} = \frac{R - Z_0}{R + Z_0} \quad (8)$$

$$R = \frac{Z_0(1 + S_{11})}{1 - S_{11}} \quad (9)$$

Then we measure the value of the resistor (shadow column) based on equation 10.

K13 $\times$ $\checkmark$ $f_x$ $=50*(1+10^{(0.1*B13)})/(1-10^{(0.1*B13)})$											
	A	B	C	D	E	F	G	H	I	J	K
13	100000000	-9.52406	3.213022	-82.1574	-69.1368	-85.4357	-63.027	0.029434	7.772037		62.55962
14	114500000	-9.55528	3.937568	-84.6159	-108.147	-75.2537	-125.471	0.020769	8.939092		62.45846
15	129000000	-9.60176	4.440008	-75.7615	149.7483	-75.8898	42.27422	0.008194	10.05047		62.30949
16	143500000	-9.63811	4.737804	-85.3826	-152.206	-81.8498	151.4072	5.04E-05	11.0617		62.19439
17	158000000	-9.60021	5.141258	-75.9402	50.57766	-86.4756	-27.5499	0.020143	12.12276		62.31445
18	172500000	-9.54529	5.510593	-73.7202	-59.3425	-80.8925	-2.95144	0.032731	13.19606		62.49074
19	187000000	-9.50509	6.182516	-84.312	16.73516	-76.5911	-29.0245	0.042096	14.32463		62.62153
20	201500000	-9.52091	7.059514	-77.3867	-162.946	-89.2959	-59.5553	0.055347	15.58054		62.56988
21	216000000	-9.58584	7.645712	-83.1544	130.705	-96.2905	-149.085	0.043833	16.71095		62.36029
22	230500000	-9.64219	7.851937	-78.8479	-11.0823	-77.2932	30.83391	0.03434	17.73884		62.18154
23	245000000	-9.64028	8.166442	-74.9536	87.05319	-73.6091	-158.632	0.036413	18.80867		62.18756
24	259500000	-9.6023	8.485704	-75.1226	-79.9839	-72.2247	-174.151	0.053805	19.84746		62.30778
25	274000000	-9.53099	9.076291	-87.6198	-178.305	-75.9748	-161.369	0.072043	20.98813		62.5371
26	288500000	-9.50915	9.693895	-84.3162	111.6014	-78.1265	-123.721	0.090413	22.20215		62.60825
27	303000000	-9.54787	10.61368	-73.1049	-97.8293	-77.2727	-149.79	0.094591	23.4481		62.48237
28	317500000	-9.63841	10.96254	-71.2097	-75.9692	-88.6694	92.63804	0.080544	24.52527		62.19344
29	332000000	-9.65102	11.23558	-81.9437	-126.636	-70.7395	-111.505	0.06987	25.57856		62.15379
30	346500000	-9.66033	11.50713	-68.4703	-43.3436	-67.263	-6.95158	0.079225	26.621		62.12462
31	361000000	-9.57656	11.82647	-77.3227	-166.366	-89.9712	108.4458	0.103221	27.65409		62.39001
32	375500000	-9.51657	12.62716	-79.8365	156.1506	-82.8279	-88.1652	0.124545	28.76952		62.58402
33	390000000	-9.52992	13.34248	-79.274	-166.028	-96.3105	173.2864	0.140906	30.03156		62.54057
34	404500000	-9.58721	14.03018	-75.3515	-157.671	-80.2852	-153.442	0.144625	31.27474		62.35591
35	419000000	-9.68303	14.30792	-78.5482	-84.621	-79.9485	-42.0291	0.139522	32.39247		62.05379
36	433500000	-9.6656	14.4929	-82.7919	122.7161	-72.2521	176.5281	0.128914	33.45513		62.10814
37	448000000	-9.63599	14.77913	-66.6762	55.953	-71.0395	171.4639	0.140904	34.5164		62.20107
38	462500000	-9.5535	15.23488	-78.3499	-155.058	-92.4228	-153.6	0.165563	35.61008		62.46419
39	477000000	-9.51086	16.1963	-97.7324	-175.213	-82.4659	-67.565	0.184324	36.75836		62.60267
40	491500000	-9.55249	16.95412	-77.4406	14.54493	-78.5571	-129.888	0.201983	38.03337		62.46744
41	506000000	-9.67139	17.55638	-81.5246	5.32927	-80.3835	-97.9055	0.196977	39.21646		62.09006
42	520500000	-9.69661	17.67423	-73.9185	70.81362	-77.8012	-114.035	0.187197	40.37915		62.01163
43	535000000	-9.69512	17.79109	-74.1617	-32.7172	-85.7047	-47.88	0.182537	41.50067		62.01627
44	549500000	-9.61303	18.11695	-78.3099	-163.718	-79.4525	-8.46142	0.208828	42.55917		62.27368
45	564000000	-9.527	18.94547	-77.5405	148.1944	-78.0451	-118.917	0.218787	43.60645		62.55004
46	578500000	-9.51852	19.6625	-79.8899	-42.2419	-75.8865	-148.808	0.247516	44.82776		62.57767
47	593000000	-9.58715	20.60423	-75.3456	-83.2462	-85.0124	86.28744	0.257535	45.96852		62.3561
48	607500000	-9.69506	20.77704	-89.144	-98.569	-75.876	-73.2698	0.25689	47.11617		62.01642
49	622000000	-9.71268	20.99672	-72.285	-24.8753	-77.5079	33.08153	0.253493	48.27071		61.96198
50	636500000	-9.6751	21.19957	-86.1563	-29.551	-87.8935	-157.419	0.270555	49.36842		62.07847
51	651000000	-9.58101	21.73474	-87.9873	20.52916	-78.0442	70.4161	0.287314	50.585		62.37574
52	665500000	-9.53858	22.56435	-82.3279	87.76836	-88.1169	-156.413	0.288464	51.70061		62.51244
53	680000000	-9.58768	23.43225	-86.4006	-23.9194	-85.5651	165.6773	0.306795	52.85875		62.35441

Figure 7: S2P data for shunt 2

WHY NOT 100!!!!!!!!!!!!!!!!!!!!!!!!!!!!

## 5 Task 5