



Engineering Assignment Coversheet

Please note that you:

- Must keep a full copy of your submission for this assignment
- Must staple this assignment
- Must NOT use binders or plastic folders except for large assignments

Student Number(s)
807739
781508
814979

Group Code (if applicable):

Assignment Title:	Workshop 3
Subject Number:	ELEN 90062
Subject Name:	High Speed Electronics
Student Name:	Xuetong Wu , Zhaoxuan Huang, Shiyu Wang
Lecturer/Tutor:	Workshop Time: Tuesday 11:00 - 1:00
Due Date:	14/09/2018

For Late Assignments Only

Has an extension been granted? Yes / No (circle)

A per-day late penalty may apply if you submit this assignment after the due date/extension. Please check with your Department/coordinator for further information.

Plagiarism

Plagiarism is the act of representing as one's own original work the creative works of another, without appropriate acknowledgment of the author or source.

Collusion

Collusion is the presentation by a student of an assignment as his or her own which is in fact the result in whole or in part of unauthorised collaboration with another person or persons. Collusion involves the cooperation of two or more students in plagiarism or other forms of academic misconduct.

Both collusion and plagiarism can occur in group work. For examples of plagiarism, collusion and academic misconduct in group work please see the University's policy on Academic Honesty and Plagiarism:
<http://academichonesty.unimelb.edu.au/>

Plagiarism and collusion constitute cheating. Disciplinary action will be taken against students who engage in plagiarism and collusion as outlined in University policy. Proven involvement in plagiarism or collusion may be recorded on my academic file in accordance with Statute 13.1.18.

STUDENT DECLARATION

Please sign below to indicate that you understand the following statements:

I declare that:

- This assignment is my own original work, except where I have appropriately cited the original source.
- This assignment has not previously been submitted for assessment in this or any other subject.

For the purposes of assessment, I give the assessor of this assignment the permission to:

- Reproduce this assignment and provide a copy to another member of staff; and
- Take steps to authenticate the assignment, including communicating a copy of this assignment to a checking service (which may retain a copy of the assignment on its database for future plagiarism checking).

Student signature  Date 14/09/2018



THE UNIVERSITY OF

MELBOURNE

UNIVERSITY OF MELBOURNE

ELEN90062 HIGH SPEED ELECTRONICS
WORKSHOP

**Workshop 3&4 Report
Calibration and Measurement**

Xuetong WU 807739
Zhaoxuan HUANG 781508
Shiyu WANG 814979

September 9, 2018

Contents

1 Calibration	2
1.1 Task 1	2
1.2 Task 2	3
1.3 Task 3	4
1.4 Task 4	7
1.5 Task 5	10
2 Matching	11
2.1 Task 1	11
2.2 Task 2	11
2.3 Task 3	15
2.3.1 Question I	15
2.3.2 Question II	15
2.3.3 Question III	15
2.4 Task 4	16
2.4.1 Question I	16
2.4.2 Question II	17
2.4.3 Question III	17
2.5 Task 5	18
2.5.1 Question I	18
2.5.2 Question II	20
2.5.3 Question III	21

1 Calibration

Executive Summary

The objective of this workshop is to calibrate the vector network analyser (VNA) and use the calibrated VNA to measure the unknown shunt for its S-parameters. The calibration is based on Short, Open, Load and Through calibration circuit board. Finally, the unknown shunt can be found by calculating its S-parameters for its impedances.

1.1 Task 1

Now we have a two port network as follows:

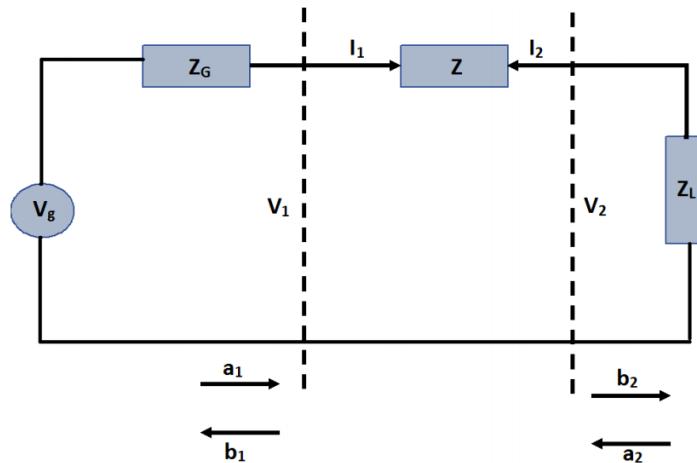


Figure 1: Two Port Network

Where a_1 and a_2 are input waves while b_1 and b_2 are defined as reflected waves, we have the equations:

$$\begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 \end{aligned}$$

And the S-parameters are defined as:

$$\begin{aligned} S_{11} &= \frac{b_1}{a_1} \Big|_{a_2=0} & S_{12} &= \frac{b_1}{a_2} \Big|_{a_1=0} \\ S_{21} &= \frac{b_2}{a_1} \Big|_{a_2=0} & S_{22} &= \frac{b_2}{a_2} \Big|_{a_1=0} \end{aligned}$$

Where S_{11} is the input reflection coefficient, S_{12} is the forward transmission gain, S_{21} is the reverse transmission gain and S_{22} is the output reflection coefficient. And for a_i and

b_i , we can show that:

$$a_i = \frac{V_i + I_i Z_0}{2\sqrt{Z_0}}$$

$$b_i = \frac{V_i - I_i Z_0}{2\sqrt{Z_0}}$$

In task 1, we consider the two-port network shown in the above, here, $Z_G = Z_0$, $Z = 0$, we can calculate the S_{11} :

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

Where:

$$b_1 = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}}, a_1 = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}}$$

Hence:

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0} = \frac{V_1 - I_1 Z_0}{V_1 + I_1 Z_0} = \frac{\frac{V_1}{I_1} - Z_0}{\frac{V_1}{I_1} + Z_0}$$

As $Z = 0$:

$$\frac{V_1}{I_1} = Z_L + Z = Z_L$$

Finally, we reach:

$$S_{11} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

1.2 Task 2

Similar to **Task 1**, S_{21} is defined as:

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

Where:

$$b_1 = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}}, a_1 = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}}$$

In this case, $Z_G = Z_0$, $Z \neq 0$, then:

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \frac{V_2 - I_2 Z_0}{V_1 + I_1 Z_0}$$

From the voltage-current relationship, we have:

$$V_2 = -I_2 Z_L$$

$$V_1 = I_1(Z_L + Z)$$

By substituting V_1 and V_2 , we reach:

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \frac{V_2 - I_2 Z_0}{V_1 + I_1 Z_0} = \frac{-I_2(Z_L + Z_0)}{I_1(Z_0 + Z + Z_L)}$$

As $I_1 = -I_2$, and if $Z_L = Z_0$, the result will be:

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \frac{V_2 - I_2 Z_0}{V_1 + I_1 Z_0} = \frac{-I_2(Z_L + Z_0)}{I_1(Z_0 + Z + Z_L)} = \frac{Z_L + Z_0}{Z_0 + Z + Z_L} = \frac{2Z_0}{Z + 2Z_0}$$

1.3 Task 3

Due to the storage error, we did not save the measurement result to the correct usb disk, hence we do not have the measurement results, to explain the calibration clearer, we use matlab to draw Smith Chart to simulate the measurement results.

For the short circuit, when calibrated, the source and load impedance should be both 0, by this the S_{11} and S_{22} can be calculated as:

$$S_{11} = \frac{Z_S - Z_0}{Z_S + Z_0} = -1$$

$$S_{22} = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

With full reflection and infinite through load, the transmission coefficients S_{12} and S_{21} should be 0, thus they are in the center point in the Smith Chart. The measurement result is as follows:

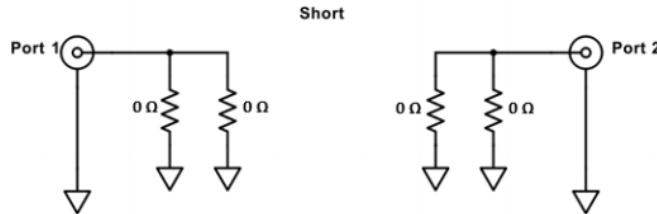


Figure 2: Short Circuit

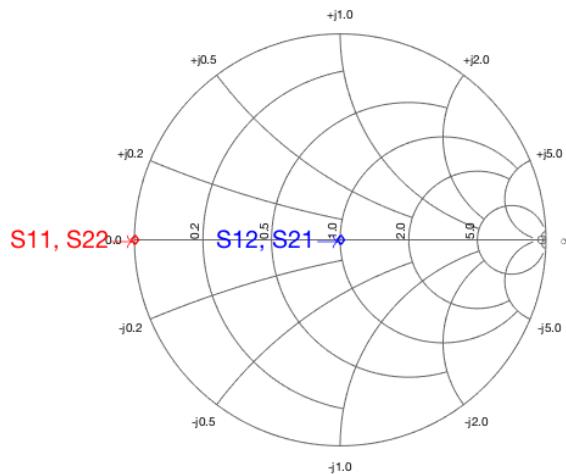


Figure 3: Short Circuit Calibration Result

Thus in the Smith Chart, S_{11} and S_{22} should be approximately at $(-1, 0)$ while S_{11} and

S_{22} locate at $(0, 0)$.

Also for the open circuit, when calibrated, the source and load impedance should be both infinite, by this the S_{11} and S_{22} can be calculated as:

$$S_{11} = \frac{Z_S - Z_0}{Z_S + Z_0} = 1$$

$$S_{22} = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$

With full reflection and infinite through load, the transmission coefficients S_{12} and S_{21} should be 0, thus they are in the center point in the Smith Chart.

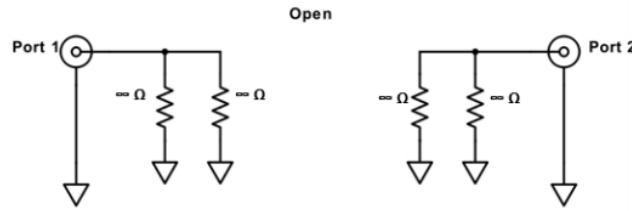


Figure 4: Open Circuit

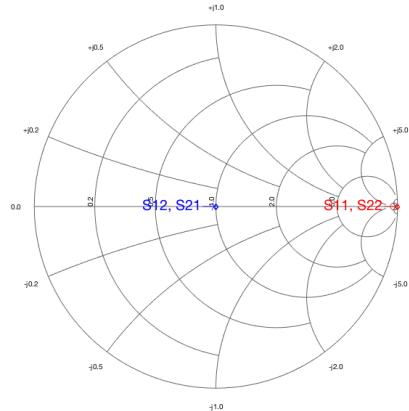


Figure 5: Open Circuit Calibration Result

Thus in the Smith Chart, S_{11} and S_{22} should be approximately at $(1, 0)$ while S_{11} and S_{22} locate at $(0, 0)$.

For load circuit, as shown as follows:

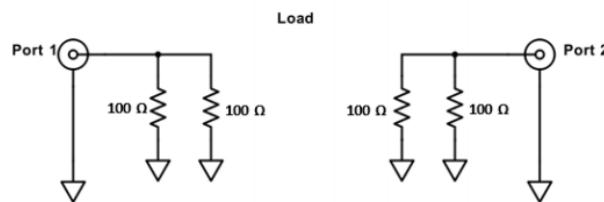


Figure 6: Load Circuit

The equivalent source impedance and load impedance are:

$$Z_S = Z_L = (100//100)\Omega = 50\Omega, Z = \infty$$

Hence:

$$S_{11} = \frac{Z_S - Z_0}{Z_S + Z_0} = 0$$

$$S_{22} = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

$$S_{21} = S_{12} = \frac{2Z_0}{Z + 2Z_0} = 0$$

In this case, all calibration S-parameters are in the center of the Smith Chart.

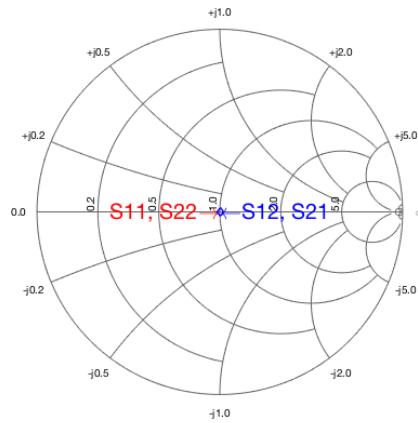


Figure 7: Load Circuit Calibration Result

Finally, we take a look at through circuits:

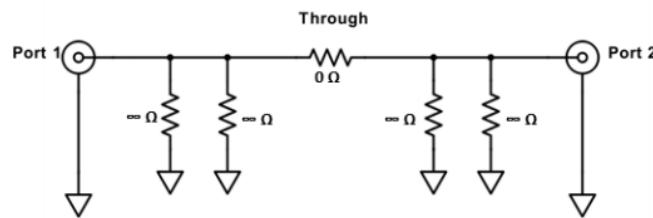


Figure 8: Through Circuit

The equivalent source impedance and load impedance are:

$$Z_S = Z_L = \infty\Omega, Z = 0$$

Hence:

$$S_{11} = \frac{Z_S - Z_0}{Z_S + Z_0} = 1$$

$$S_{22} = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$

$$S_{21} = S_{12} = \frac{2Z_0}{Z + 2Z_0} = 1$$

In this case, all calibration S-parameters are located at (1, 0) of the Smith Chart.

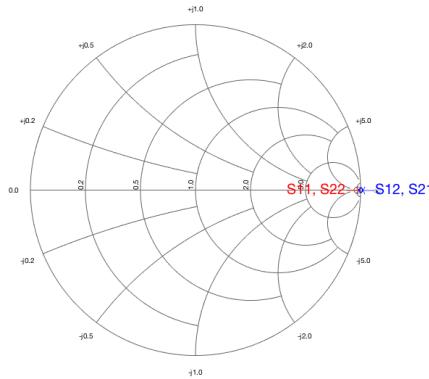


Figure 9: Through Circuit Calibration Result

1.4 Task 4

We have two unknown shunt circuits, as it is single port, we only care about the **reflection coefficient** S_{11} as it is:

$$S_{11} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

At 500MHz, by reading the *s2p* data, here the format for *.s2p* files are: in **.s2p* files each record contains 1 frequency value and 4 S-parameters (total of 9 values), just before the data section of an *s2p* file, there should be a line that looks like this:

Hz S DB R 50

Here, *Hz* means the operating frequency, *S* means *S*-Parameter, *DB* stands for the unit of the value(decibel/angle), and *R 50* indicates that the load impedance is 50Ω . And for the 9 values, they represent:

Frequency, Magnitude(S_{11}), Phase(S_{11}), Magnitude(S_{21}), Phase(S_{21}), Magnitude(S_{12}), Phase(S_{12}), Magnitude(S_{22}), Phase(S_{22})

The table looks like below:

```

1 !Agilent N9914A: A,06,08
2 !Date: Tuesday, 28 August 2018 11:26:44
3 !Model: N9914A
4 !Serial: MY52401119
5 !GPS Latitude:
6 !GPS Longitude:
7 !GPS TimeStamp: 0001-01-01 00:00:00Z
8 !GPS Seconds Since Last Read: 0
9 !S11: 0.9608<-90.49dB
10 !Correction: S11(ON US12(ON US12(ON US12(ON U)
11 !SP2 File: Measurements.S11,S21,S12,S22;
12 # Hz S DB R 50
13 0.0000000 -0.216455139189567 -78.1272911829676 -78.1301347295467 163.458252503173 -86.4186612384291 -154.853913353197 0.043932947336286 10.371382882547
14 1145000000 -0.224493982885132 -72.8590834064095 -88.409940661493 188.1894079428817 -81.2846137936345 -50.4184918392639 -0.077414895996571 12.0986463243961
15 1290000000 -0.224493982885132 -72.8590834064095 -88.409940661493 148.969169296453 -78.43166392763 -56.563775157163 -0.031757195697968 13.6267568623943
16 1435000000 -0.2378584198512 -28.1310886385308 -75.063751684775 30.1298669186477 -77.739119670625 -30.6813986924582 -0.064851867915112 14.8994439597142
17 1580000000 -0.2523084198512 -28.1310886385308 -75.063751684775 30.1298669186477 -77.739119670625 -30.6813986924582 -0.064851867915112 14.8994439597142
18 1725000000 -0.2668584198512 -34.7074924612842 82.338632247053 -94.6538633164633 -78.6591942187053 144.89955387965 -0.0164346336639301 17.46621977009
19 1870000000 -0.019017083158519 -37.2351298862821 82.334733824684 28.1217581163642 -72.748927316975 -21.3559606150202 0.032136397201008 18.0317088883316
20 2015000000 -0.0922844728480877 88.730972846162 -70.312984181167 148.6863624670994 -88.7753202174373 173.1132549514202 0.0542361185398822 20.8577475861111
21 2160000000 -0.194823979797151 -42.2735450586283 59.02864522883322 151.322122883322 -78.332773670544 88.7753202174373 173.1132549514202 0.0542361185398822 20.8577475861111
22 2305000000 -0.20938061230202 -48.988347490521 74.6266251908317 -74.7870511226197 -136.934237616718 0.058242588133 -0.02649214894670062
23 2450000000 -0.231293527996928 -48.988347490521 74.6266251908317 -74.7870511226197 -136.934237616718 0.058242588133 -0.02649214894670062
24 2595000000 -0.1584255786273736 -50.824563709464 -79.9058415983866 -1.3594698215733 -88.3751673407962 -0.02649214894670062
25 2740000000 -0.053436366918576 -53.3868128434838 -81.8393529854876 -19.798816773399 -91.3896189160772 92.0698580243876 0.0262836492333156 27.9589553855288
26 2885000000 -0.1962041721278453 -57.886954381138 -78.4360279548479 -140.2231962571 -77.049434515817 154.570968982829 0.072617826479846 31.0315775285231
27 3030000000 -0.1962041721278453 -57.886954381138 -78.4360279548479 -140.2231962571 -77.049434515817 154.570968982829 0.072617826479846 31.0315775285231
28 3175000000 -0.293525845508799 -60.0573665051842 -78.8334978178423 39.3641084786765 -71.16182435262189 -48.5622083380617 0.023659856532874 32.642237188866
29 3320000000 -0.293525845508799 -60.0573665051842 -78.8334978178423 39.3641084786765 -71.16182435262189 -48.5622083380617 0.023659856532874 32.642237188866
30 3465000000 -0.153877277434436 -68.462587615095 -68.147172256667 -137.45628339694 -79.526766189942 166.161799177956 -0.0011194480181124 36.74947282738
31 3610000000 -0.153877277434436 -68.462587615095 -68.147172256667 -137.45628339694 -79.526766189942 166.161799177956 -0.0011194480181124 36.74947282738
32 3755000000 -0.134939971701595 -70.7112015521091 96.2387991965586 -96.2387991965586 -79.4719742299583 113.395989135724 0.0527686498191869 38.13768396911131
33 3900000000 -0.208997723849344 -73.8050087614212 -81.9787318511783 -82.078255111264 33.76973362767076 0.092892786332412 39.728739853275
34 4045000000 -0.30834754299284 -75.1172712039719 76.87854952285784 -74.8674931641999 7.2245428866471 0.0696352934729575 31.485436589724
35 4190000000 -0.349596841538748 -80.4268251908317 -80.4268251908317 -83.502825857807 17.2591281165027 -0.0143599683914 44.128652873986
36 4335000000 -0.292933469132828 -88.0824951266467 -88.0824951266467 -83.502825857807 17.2591281165027 -0.0143599683914 44.128652873986
37 4480000000 -0.203499911230873 -82.1328916156577 -84.573258337354 173.49003433364 -130.058967565763 -0.0032378313297399 45.4147972784635
38 4625000000 -0.165596160847933 -84.3039936414831 -84.1447094188213 124.21138028697 -79.7615137281513 81.7171259999933 0.054768552575737 46.847178599595
39 4770000000 -0.165596160847933 -84.3039936414831 -84.1447094188213 124.21138028697 -79.7615137281513 81.7171259999933 0.054768552575737 46.847178599595
40 5115000000 -0.292951844652459 -88.1169823754934 -88.1169823754934 -88.1169823754934 -174.623774984531 -77.995984198767 149.02987369248 0.122920838540825 58.0873393819268
41 5660000000 -0.347295742258749 -88.1169823754934 -88.1169823754934 -88.1169823754934 -181.631843222454 -88.1169823754934 -88.1169823754934 -0.09067674231043 51.561254828664
42 5805000000 -0.345968941538748 -92.3889968416913 -76.0043878792645 -76.0043878792645 -175.07205929393 0.04967784472 0.03192873898649 52.88638270383
43 5950000000 -0.283012785369994 -77.752871254667 -79.748511897844 -79.748511897844 -118.367256288994 -0.0859347764919823 54.1841661074023
44 5955000000 -0.29263107339772 -96.4149298435308 -71.3642596256314 -81.0873846153149 -146.66415311649 0.0116440970996734 55.361153334767

```

Figure 10: *sp2* format for unknown circuit 1

we can find the according frequency response at a certain frequency. For the unknown shunt circuit 1, the nearest value to the target frequency is 506MHz, and for S_{11} :

$$S_{11,dB} = -0.3472dB \Rightarrow 20 \log(|S_{11}|) = -0.3472dB \Rightarrow |S_{11}| = 0.9608$$

$$S_{11,angle} = -90.49^\circ$$

Thus $S_{11} = 0.9608 \angle -90.49^\circ$, which is equivalent to:

$$S_{11,Re} = -0.0082$$

$$S_{11,Im} = -0.9607j$$

The characteristic impedance is 50Ω , therefore, we can compute the load impedance:

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} Z_0 = \frac{1 + S_{11}}{1 - S_{11}} Z_0 = (1.9848 - 49.5356j)\Omega$$

The trace of S-parameter in dB is as follows:

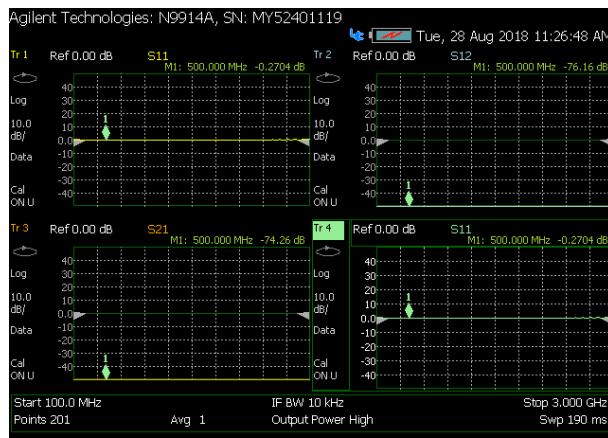


Figure 11: S-parameter display for unknown circuit 1

For unknown shunt 2, we have:

5	IGPS Latitude:
6	IGPS Longitude:
7	IGPSTimeStamp: 0001-01-01 00:00:00Z
8	IGPS Seconds Since Last Read: 0
9	I_CHECKSUM:1109555246
10	Correction: S11(ON U)S21(ON U)S12(ON U)S22(ON U)
11	ISZP File: Measurements:S11,S21,S12,S22:
12	# Hz S DB R 50
13	-9.38111382669657 2.646282592788694 -76.495903309521 -148.625237680477 -88.1266256628798 -113.450512688857 0.045285242282092 10.3722522300059
14	-9.4456747788452 3.87747921673288 -69.592217197591 23.729284676214 -77.619412072587 -156.55914768157 0.078703236448464 12.6982432369824
15	-9.62959362082865 4.25902951619723 -98.2703858282063 -154.702833611962 -74.423594428007 42.3064266000498 0.042183712437013 13.6932267690988
16	-9.69603236667984 3.8846517237246 -83.909276402555 -116.50994572233 -81.3768977323272 139.688288344994 -0.075630230475731 14.8431821649124
17	-9.6362414367742 3.4781546588998 -87.848425792494 -17.688576019807 -73.1320826463927 171.655117789538 -0.0483000776921065 16.0957536460812
18	-9.46196364411892 3.631961122777004 -77.2018131190855 -42.004343460946 -77.2068332990118 116.4580228479716 -0.0262870791512594 17.338263175544
19	-9.361522895347493 6.07836041403322 -85.2430362186218 -65.3001487436261 -79.0399149418874 66.7321669703324 0.05663374901873404 20.8332841968859
20	-9.361512895754627 6.07836041403322 -85.2430362186218 -65.3001487436261 -79.0399149418874 66.7321669703324 0.05663374901873404 20.8332841968859
21	-9.50917400534318 6.05911260824169 -79.1054748529456 -117.095746230089 -83.19861797555783 144.476230272648 0.025241319677772 22.4900554279807
22	-9.68518954376473 6.1981450004668 -76.1418160110841 -169.789930494448 -80.0636179437476 112.862575187096 -0.039555053556332 24.0200148515264
23	-9.245000000000000 6.47828708163601 -83.5321957337493 -7.43734727954518 -77.9321717861737 178.31398327275 -0.06068977993574199 25.3678573741669
24	-9.56896316134164 6.08586317423209 -78.0887047225337 -97.51378457083886 -173.2216510710931 -0.0318915815384916 26.5714864009448
25	-9.3946834693247 6.82359667927615 -78.3991444136899 -43.4747513511323 -82.3881734328484 -16.8585337403369 0.07635646070185647 27.9976714328677
26	-9.31041749920157 8.26987213323143 -85.6702996705485 -9.00332025525208 -82.889731390528 -74.2524862000000 0.06967732046791594 29.635438738554
27	-9.500360000000000 9.46028708163601 -76.1418160110841 -169.789930494448 -80.0636179437476 10.29404427711422 -0.023797733970533 30.397132043063
28	-9.6843993696604 8.8984651721798 -82.6959293315777 -47.5308677448084 -73.799761676431 94.2390002684037 0.024474057602224 32.8186287663306
29	-9.75285428313731 9.54903478173947 -71.8235562837712 -68.9122733929579 -75.30664978335781 -60.989049876462 0.0291046221443439 34.39377921959
30	-9.332000000000000 6.852192964533771 -79.6562282246661 -104.727157769362 -75.0791166326422 111.9152621851555 -0.0451219891997855 35.7498257576798
31	-9.361000000000000 9.4769887898896 9.0382308288027 -84.3021881221441 -55.7282512157098 -80.5227819599797 128.73206496869 -0.0134149880714743 36.9853887788899
32	-9.375500000000000 9.33026056858866 -77.32009850386331 -84.2670456486275 146.3141524411959 0.0525989974367816 38.2468522412669
33	-9.390000000000000 9.3362858777333 11.6328623095373 -75.2424851829552 73.5542332399233 -86.7448771911942 -177.868279816145 0.097853256221974 39.770671490793
34	-9.54097489211165 12.9859009501203 -75.42570283323542 92.6621393547249 -88.5452325579471 -146.248120120829 0.0678078186156558 41.4687328013613
35	-9.7288305743893 12.9975681315274 -81.5397744369318 -118.1281722443 -81.0355623145993 34.446601230278 0.01962250570140428 42.8667118241846
36	-9.79824146971529 12.9975681315274 -81.5397744369318 -118.1281722443 -81.0355623145993 79.0125700485026 -0.0269295014711464 44.1861421624308
37	-9.634800000000000 12.9975681315274 -81.5397744369318 -118.1281722443 -81.0355623145993 -118.256735616847 -0.0159697840131567 45.498588922609
38	-9.462500000000000 9.438268717398363 -88.0424265783195 -52.931685704161708 -80.1225143822281 -174.867947569143 0.0481013696213539 46.8930313103795
39	-9.437000000000000 9.287044496477 14.9181444711046 -86.45504611047 -63.0891282360181 -76.7512122646768 -114.73480765917 0.12820003691127 50.0574194330996
40	-9.437000000000000 9.287044496477 14.9181444711046 -86.45504611047 -63.0891282360181 -76.7512122646768 -114.73480765917 0.12820003691127 50.0574194330996
41	-9.560000000000000 15.8097500007969 -75.40907247238 -7.249599306538290 -76.2954205415983 125.3020214941 0.095516795667803 51.4975003674696
42	-9.520000000000000 9.76762426795857 7.7121241915971 -77.060755516667 -147.7572727392881 -73.7676597125422 0.0937517014829 0.0337180878649002 52.8178294989252
43	-9.535000000000000 9.777960571996055 14.7884591228728 -82.-9576953742341 -16.671468728016 -81.0639970191371 62.8924406724333 -0.0166671979499229 54.11787626265935
44	-9.549500000000000 9.5715396318773 -73.483394449222 -103.958824508366 -78.0230702739506 78.1788698048671 0.02575552896826111 55.3382174913842
45	-9.564000000000000 15.30173817606247 -85.6316207617862 -46.131748936408 -74.678819472361 168.354232738109 0.0762678302679277 56.896379894193
46	-9.578500000000000 9.34064346109469 -84.3798147849252 -23.6153966065491 -84.3418025636824 -106.0686668351289 0.140474868737101 58.6103853994843
47	-9.593000000000000 9.49157357395777 18.3862538304396 -77.5335812848967 -25.8660295001026 -88.1615724726433 97.1449977007644 0.153353031589426 60.160646056601
48	-9.607500000000000 9.66683094340796 18.832676401724 -81.0817394672304 -164.412797259849 -78.0053995139121 0.107625453972071 61.722594480297

Figure 12: sp2 format for unknown circuit 2

From the table, yielding:

$$S_{11,dB} = -9.615dB \Rightarrow 20 \log(|S_{11}|) = -9.615dB \Rightarrow |S_{11}| = 0.33$$

$$S_{11,angle} = 15.9^\circ$$

Thus $S_{11} = 0.33\angle 15.9^\circ$, which is equivalent to:

$$S_{11,Re} = 0.3174$$

$$S_{11,Im} = 0.09j$$

The characteristic impedance is 50Ω , therefore, we can compute the load impedance:

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} Z_0 = \frac{1 + S_{11}}{1 - S_{11}} Z_0 = (93.97 + 19.07j)\Omega$$

The trace of S-parameter in dB is as follows:

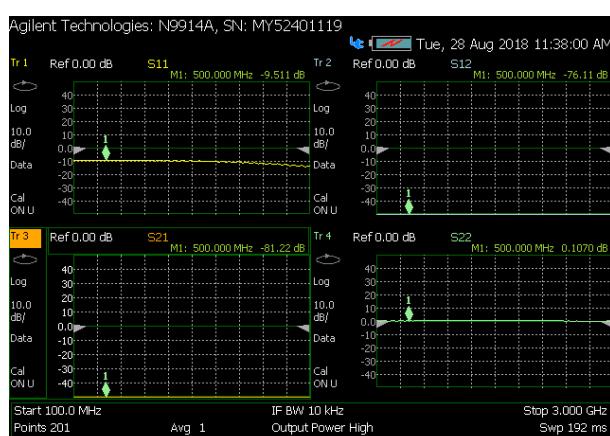


Figure 13: S-parameter display for unknown circuit 2

1.5 Task 5

Based on the *s2p* file, the record values are shown in the figure below:

```

!Agilent N9914A: A.06.08
!Date: Tuesday, 28 August 2018 11:29:47
!Model: N9914A
!Serial: MY52401119
!GPS Latitude:
!GPS Longitude:
!GPS Altitude:
!GPS Seconds Since Last Read: 0
!CHECKSUM: 0636978779
!Correction: S11(ON U)S12(ON U)S22(ON U)
!S2P File: Measurements:S11,S21,S12,S22:
# Hz S DB R 50
100000000 -26.2541699619754 78.4395595270556 -0.0697796046567847 -1.5085265560184 -0.097511979197524 -1.62399428768586 -25.8146988558496 71.7147680942003
114500000 -24.418879941698 79.973148873763 -0.0710465181019 -1.83860469111 -0.1174625357733 -1.9863181576733 -23.147819385539 79.9383426595280
120000000 -22.316483082941 80.11860469111 -0.0805579855932 -2.2913660469111 -0.108252265560184 -2.3913660469111 -22.37747819385539 79.70875414148
143500000 -22.316483082941 86.8123898656977 -0.0918680288023368 -2.627114494512114 -0.1117367902987 -2.627114494512114 -21.191018941447 84.8479837544148
158000000 -21.5808797789483 87.66825264119 -0.088235705282899 -2.98740064316748 -0.114509807135701 -3.0007573549397 -22.895991639164 85.674267828996
172500000 -20.803051484888 85.6521431762121 -0.05878643265679 -3.17025172565638 -0.0829651671713342 -3.17478158007083 -21.3896611342314 85.7387652271934
187000000 -19.8996492477217 84.224564597221 -0.065414159364885 -3.3449893776828 -0.0875403116258417 -3.42981431974968 -20.365913621127 88.2949328757148
201500000 -18.910269426671 83.4814624589986 -0.0935531381761931 -3.5775310355837 -0.121496367477945 -3.71468242183952 -19.0274776995164 88.969694593562
216000000 -18.2271685317651 84.44576424808696 -0.11526408618684 -3.94858370545887 -0.1456101934134844 -3.84683613377245 -18.2699574992929 85.1836463393653
230500000 -17.77178663377722 85.1223898656977 -0.14900854152413 -4.68902754862854 -0.1780830320441 -4.51890830320441 -17.77178663377722 85.751499355471
245000000 -17.73161429522941 85.6462566914213 -0.142437437441534 -4.32389487443772 -0.1780830320441 -4.116189192933 -17.73161429522941 85.8613991380134
259500000 -17.0020522208508 84.363636192946 -0.13581847152631 -4.92711897983616 -0.16007754862854 -0.16007754862854 -17.5452718335997 85.9205213191691
274000000 -16.4401789789011 82.7775637814641 -0.124941185335287 -5.0452454896528 -0.152179183017799 -0.152179183017799 -16.8931128018132 81.5027857359872
288500000 -15.8638811024476 82.0450832174961 -0.14581585261753 -5.21510114173212 -0.176255015270333 -5.05001428013691 -16.8822836759988 80.2928296250262
303000000 -15.3424582976647 82.48367648480533 -0.172851247082939 -5.4928118892859 -0.19946747989057 -5.51841438765958 -15.5479888757582 81.5600866709161
317500000 -14.95364762980811 83.413470163118 -0.20394342735518 -5.85591012768486 -0.230157531538507 -5.94482129812982 -15.124940146217 84.8350146378497
332000000 -14.7351164252257 83.89297502118 -0.23523784475559 -6.2542586678397 -0.25707753694856 -6.3043425377086 -14.9149661836184 86.921459428735
346500000 -14.595581330729 83.10915718205 -0.22338741929205 -6.780414994513193 -0.2390791361185 -6.80211808958685 -0.2409462419995161 -8.396779542531
352000000 -14.105581330729 83.1740741260467 -0.23576044335932 -6.780414994513193 -0.2390791361185 -6.80211808958685 -0.2409462419995161 -8.396779542531
375500000 -13.6969313499663 80.844066787358 -0.218703154379374 -6.785237726565677 -0.23752431862514 -6.80507182882845 -0.2409462419995161 -8.396779542531
390000000 -13.2752327659348 80.6669427110571 -0.235618584545877 -6.98428465536531 -0.258973813832112 -6.99514519464587 -0.269630742197102 -7.2801542138956 -13.1424725044779 82.1832915988307
404500000 -12.9664022323843 81.8469359857411 -0.284646194377014 -7.25798699536733 -0.309630742197102 -7.2801542138956 -13.1424725044779 82.1832915988307
419000000 -12.8138110853355 82.2247931882235 -0.311140688346172 -7.75105939316054 -0.338811991887813 -7.75422888998538 -12.9917729623279 83.9838631274599
433500000 -12.6693367281181 82.1901567396018 -0.327529634378954 -8.9670987865444 -0.34524797659717 -8.1315698999595 -12.9722425267222 84.1209883835606
448000000 -12.4258636583338 81.0119497975381 -0.317390391530249 -0.317390391530249 -0.3369352662407 -0.33615383130149 -12.8397683637591 81.75545053948
462500000 -12.2089067277188 79.72351785920228 -0.327529634378954 -8.9670987865444 -0.34524797659717 -8.1315698999595 -12.9722425267222 84.1209883835606
477000000 -11.720868235307 79.3712864456322 -0.329682462266085 -0.349106947188948 -0.425844205648952 -0.428872886550292 -0.435834123577589 -0.435834123577589 -11.774286548952 -78.210617811642
491500000 -11.4090914398803 79.0825331036804 -0.363615576439815 -0.733652377234814 -0.81412624599387 -0.81412624599387 -11.6062233265799 80.3685740891836
506000000 -11.2028431041614 79.9319251455592 -0.409570655482585 -0.66612700997362 -0.428872886550292 -0.4358972393610342 -0.46525800160771 -0.46525800160771 -11.3358972393610342 -81.5749559526049
520500000 -11.0809067277188 80.2351785920228 -0.430675403923504 -0.36581493304827 -0.45372393610342 -0.46525800160771 -0.46525800160771 -11.2612524726571 -83.107888735363
535000000 -10.9409896684728 79.957080446907 -0.435953975677893 -9.771320631755 -0.455576071756911 -9.8107630008169 -0.458563412011919 -0.458563412011919 -11.1939667552114 79.6277193177363
549500000 -10.7088763037489 78.7012299017505 -0.43245538103465 -0.72323675094136 -0.458563412011919 -0.458563412011919 -0.458563412011919 -11.1939667552114

```

Figure 14: *s2p* format for unknown through circuit

The S-parameters of the two-port network are calculated as:

$$\begin{aligned} S_{11} &= 0.2753 \angle 79.93^\circ & S_{12} &= 0.9543 \angle -9.07^\circ \\ S_{21} &= 0.9518 \angle -9.06^\circ & S_{22} &= 0.2713 \angle 81.57^\circ \end{aligned}$$

From $S_{21} = \frac{2Z_0}{Z+2Z_0}$, we can calculate:

$$S_{21} = \frac{100}{Z + 100} = 0.9518 \angle -9.06^\circ$$

$$\Rightarrow Z = \frac{2Z_0}{S_{21}} - 2Z_0 = (3.7534 + 16.5438j)\Omega$$

As a result, the through load is $(3.7534 + 16.5438j)\Omega$.

2 Matching

Executive Summary

The objective of this lab is to use two-port characteristics to design a microwave amplifier to find the maximum gain. A single stub is used to find conjugate matching to maximum the gain. In this lab, two approaches are applied, hand calculation and CST simulation, and the results of both are compared for verification.

2.1 Task 1

Looking from input port, we write:

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} = R_{in} + X_{in}$$

Then we reach:

$$\begin{aligned} P_L &= \frac{V_g^2 \times R_{in} \times |1 - |\Gamma_L^2|| \times |1 - |\Gamma_S^2||}{2(Z_g + Z_{in})^2} = \frac{V_g^2 \times R_{in} \times |1 - |\Gamma_L^2|| \times |1 - |\Gamma_S^2||}{2((R_g + R_{in})^2 + (X_g + X_{in})^2)} \\ \Rightarrow P_L &= \frac{V_g^2 \times R_{in} \times |1 - |\frac{(Z_L - Z_0)^2}{(Z_L + Z_0)^2}|| \times |1 - |\frac{(Z_g - Z_0)^2}{(Z_g + Z_0)^2}||}{2((R_g + R_{in})^2 + (X_g + X_{in})^2)} \end{aligned}$$

By this we try to minimise the denominator of P_L :

$$\min(2((R_g + R_{in})^2 + (X_g + X_{in})^2))$$

Hence, let $X_g = -X_{in}$ to reduce the effect of reactance, the load power becomes:

$$P_L = \frac{V_g^2 \times R_{in} \times |1 - |\frac{(Z_L - Z_0)^2}{(Z_L + Z_0)^2}|| \times |1 - |\frac{(Z_g - Z_0)^2}{(Z_g + Z_0)^2}||}{2((R_g + R_{in})^2)} = \frac{V_g^2 \times |1 - |\frac{(Z_L - Z_0)^2}{(Z_L + Z_0)^2}|| \times |1 - |\frac{(Z_g - Z_0)^2}{(Z_g + Z_0)^2}||}{2(R_{in} + \frac{R_g^2}{R_{in}} + 2R_g)}$$

P_L reaches max when $R_{in} = R_g$, as a result, when:

$$R_{in} = R_g, X_g = -X_{in} \Rightarrow Z_{in} = Z_g^*$$

P_L is maximized.

2.2 Task 2

From the conjugating conditions, we can explicitly derive solutions for Γ_S and Γ_L :

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4C_1^2}}{2C_1}$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4C_2^2}}{2C_2}$$

Where:

$$\begin{aligned} B_1 &= 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ B_2 &= 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_1 &= S_{11} - \Delta S_{22}^* \\ C_2 &= S_{22} - \Delta S_{11}^* \\ \Delta &= S_{11}S_{22} - S_{12}S_{21} \end{aligned}$$

In this question, the S parameters for a BJT at **2.4GHz** is:

$$\begin{aligned} S_{11} &= 0.912\angle 127.1^\circ \\ S_{11} &= 0.041\angle 26.0^\circ \\ S_{11} &= 1.721\angle 35.6^\circ \\ S_{11} &= 0.75\angle 143.9^\circ \end{aligned}$$

With the help of matlab, the calculation code is as followed:

```

1 %Here is the calculation of S-Parameter
2 S11 = 0.912*cos(127.1/180*pi) + 0.912*sin(127.1/180*pi)*j;
3 S12 = 0.041*cos(26/180*pi) + 0.041*sin(26/180*pi)*j;
4 S21 = 1.721*cos(35.6/180*pi) + 1.721*sin(35.6/180*pi)*j;
5 S22 = 0.75*cos(143.9/180*pi) + 0.75*sin(143.9/180*pi)*j;
6
7 %Calculation for some parameters
8 DELTA = S11*S22 - S12*S21;
9 B1 = 1 + abs(S11)*abs(S11) - abs(S22)*abs(S22) - abs(DELTA)*abs(DELTA);
10 B2 = 1 + abs(S22)*abs(S22) - abs(S11)*abs(S11) - abs(DELTA)*abs(DELTA);
11 C1 = S11 - DELTA*conj(S22);
12 C2 = S22 - DELTA*conj(S11);
13
14 %Calculation for Gamma
15 GAMMAS1 = (B1 + sqrt(B1*B1 - 4*abs(C1)*abs(C1)))/(2*C1);
16 GAMMAS2 = (B1 - sqrt(B1*B1 - 4*abs(C1)*abs(C1)))/(2*C1);
17 Gammal1 = (B2 + sqrt(B2*B2 - 4*abs(C2)*abs(C2)))/(2*C2);
18 Gammal2 = (B2 - sqrt(B2*B2 - 4*abs(C2)*abs(C2)))/(2*C2);
19
20 %Calculation for gain
21 GAMMAIN = S11 + (S12*S21*Gammal2)/(1-S22*Gammal2);
22 GT = abs(S21)*abs(S21);
23 GMAX = abs(S21)*abs(S21)*(1-abs(Gammal2)*abs(Gammal2))/((1-abs(GAMMAS2)*
    abs(GAMMAS2))*abs(1-S22*Gammal2)*S22*Gammal2));
24 Ratio = GMAX/GT;
```

Yielding the result:

$$\Gamma_L = -0.5909 - 0.1240j = 0.6038\angle -168.14^\circ$$

$$Y_L = 0.6038\angle 11.85^\circ$$

$$\Gamma_S = -0.5889 - 0.6701j = 0.8921\angle -131.31^\circ$$

$$Y_S = 0.8921\angle 48.69^\circ$$

The original transducer gain G_T is:

$$G_T = |S_{21}|^2 = 2.9618 = 4.716dB$$

Under the maximum gain with conjugate matching:

$$G_{max} = \frac{|S_{21}|^2(1 - |\Gamma_L|^2)}{(1 - |\Gamma_S|^2)(|1 - \Gamma_L S_{22}|^2)} = 24.3144 = 13.859dB$$

Which improves approximately 9.143dB.

The stub-matching for the generator can be implemented using the Smith Chart shown below:

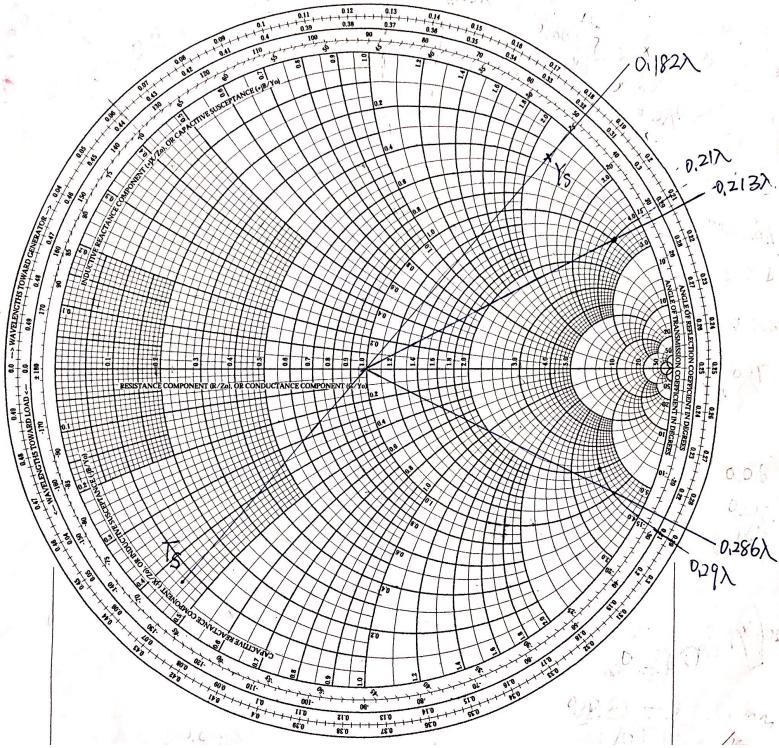


Figure 15: Stub Matching Smith Chart for generator(Γ_S)

Here, from the figure we have two solutions:

$$l_{stub,in1} = 0.21\lambda, l_{in,1} = 0.469\lambda$$

$$l_{stub,in2} = 0.29\lambda, l_{in,2} = 0.396\lambda$$

Similarly, for the load impedance matching:

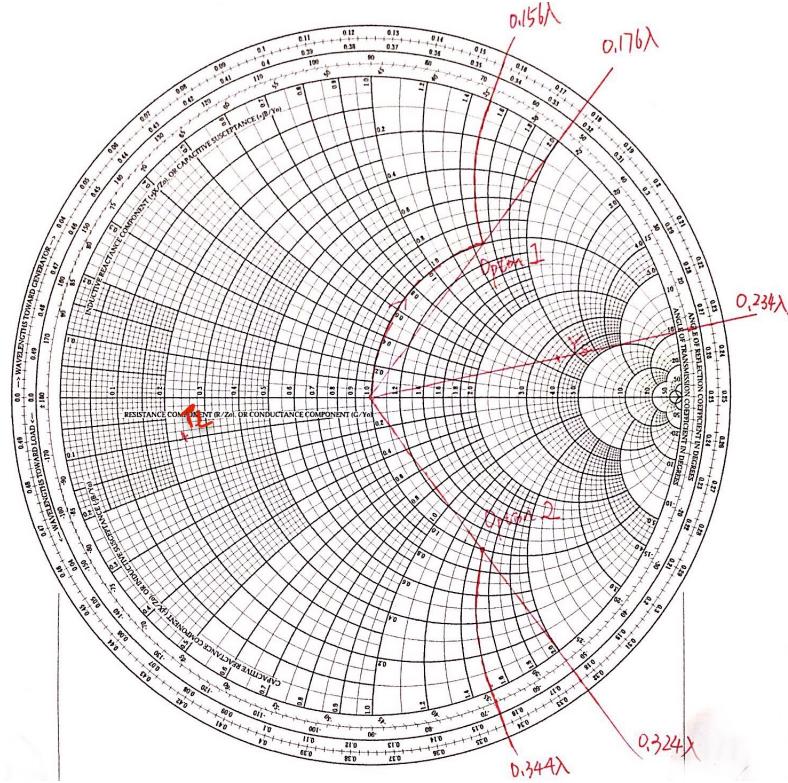


Figure 16: Stub Matching Smith Chart for load(Γ_L)

Here, from the figure we have two solutions:

$$l_{stub,out1} = 0.156\lambda, l_{out,1} = 0.058\lambda$$

$$l_{stub,out2} = 0.344\lambda, l_{out,2} = 0.41\lambda$$

The wavelength of on the strip can be calculated as:

$$\varepsilon_{eff} = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12h/W}} = 3.2623$$

$$\lambda = \frac{c}{\sqrt{\varepsilon_{eff}}f} = \frac{3 \times 10^8}{\sqrt{3.2623} \times 2.4 \times 10^9} = 69.2\text{mm}$$

Hence:

$$l_{stub,in1} = 0.21\lambda = 14.532\text{mm}, l_{in,1} = 0.469\lambda = 32.45\text{mm}$$

$$l_{stub,in2} = 0.29\lambda = 20.068\text{mm}, l_{in,2} = 0.396\lambda = 27.4\text{mm}$$

$$l_{stub,out1} = 0.156\lambda = 10.79\text{mm}, l_{out,1} = 0.058\lambda = 4\text{mm}$$

$$l_{stub,out2} = 0.344\lambda = 23.8\text{mm}, l_{out,2} = 0.41\lambda = 28.372\text{mm}$$

2.3 Task 3

2.3.1 Question I

By the simulation, the optimized micro strip width w is 2.31mm shown in the figure below:

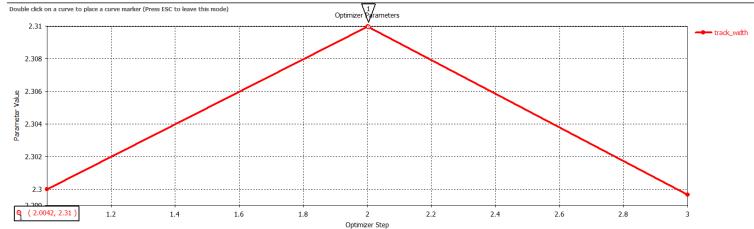


Figure 17: Optimized Microstrip Width w

And the corresponding characteristic impedance response is:

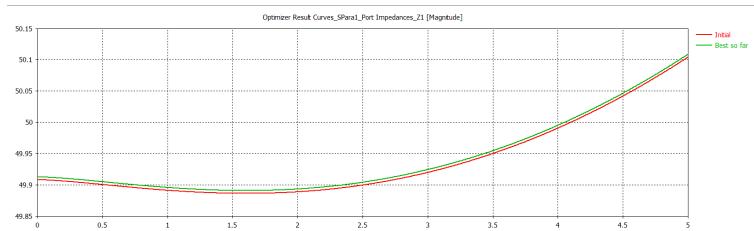


Figure 18: Optimized Microstrip Impedance Response

2.3.2 Question II

The impedance Z_0 follows the following relationship:

$$Z_0 = \frac{87}{\sqrt{\epsilon_r + 1.41}} \ln \frac{5.98h}{0.8w + T} = 50\Omega$$

Where $\epsilon_r = 4.3$, $h = 1.2\text{mm}$, $T = 35\mu\text{m}$, yielding:

$$w = 2.228\text{mm}$$

2.3.3 Question III

The calculated value $w = 2.228\text{mm}$ is a bit less than the theoretical value $w = 2.31\text{mm}$, but they are much close that we could consider almost the same, the differences are mainly caused by the simulation environment and the calculation approximation, actually the impedance of the microstrip is:

$$Z_0 = \frac{\eta_0}{2\pi\sqrt{2}\sqrt{E_r + 1}} \ln \left(1 + 4(X_1 + X_2) \left(\frac{H}{W_{eff}} \right) \right)$$

Where:

$$W_{eff} = W + \left(\frac{t}{\pi} \right) \ln \left(\frac{4e}{\sqrt{\left(\frac{T}{H} \right)^2 + \left(\frac{T}{W\pi + 1.1T\pi} \right)^2}} \right) \frac{E_r + 1}{2E_r}$$

$$X_1 = 4\left(\frac{14E_r + 8}{11E_r}\right)\left(\frac{H}{W_{eff}}\right)$$

$$X_2 = \sqrt{16\left(\frac{H}{W_{eff}}\right)^2\left(\frac{14E_r + 8}{11E_r}\right)^2 + \left(\frac{E_r + 1}{2E_r}\right)\pi^2}$$

The equation given in **Question II** is also an approximation of the characteristic impedance, hence we may put $2.3mm$ as our optimized width value.

2.4 Task 4

2.4.1 Question I

The S_{11} looking from input side(left side of the left micro strip) is:

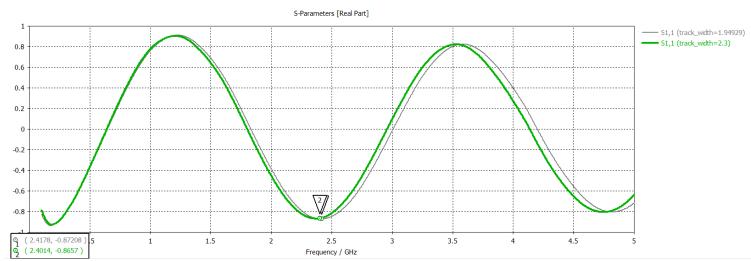


Figure 19: Real Part of S_{11}

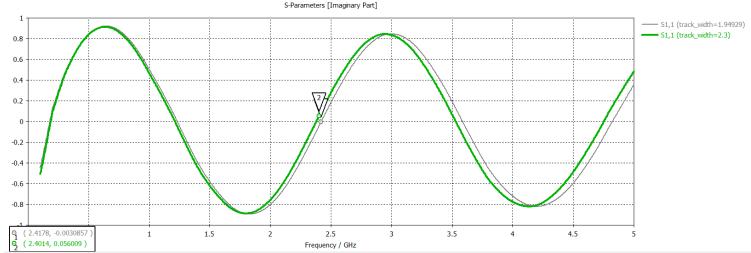


Figure 20: Imaginary Part of S_{11}

Hence:

$$S_{11} = -0.8657 + 0.056j = 0.8675\angle176.2988^\circ$$

The S_{22} looking from right side(right side of the right micro strip) is:

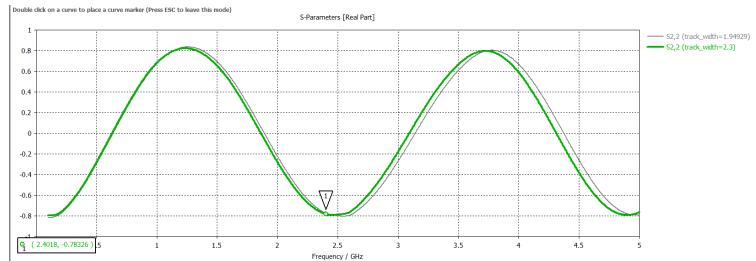
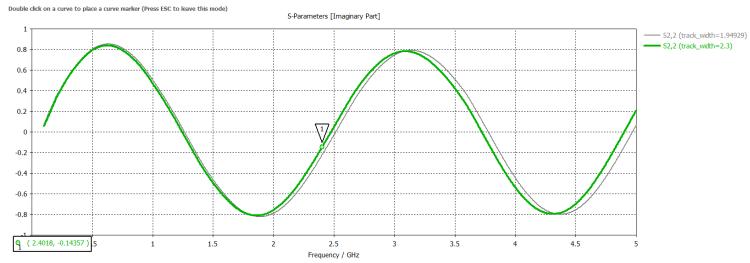


Figure 21: Real Part of S_{22}

Figure 22: Imaginary Part of S_{22}

Hence:

$$S_{22} = -0.7833 - 0.14357j = 0.7963\angle -169.6^\circ$$



2.4.2 Question II

As the impedance of the source and load is matched, the gain of the amplifier is:

$$G_T = |S_{21}|^2 = 1.3842^2 = 1.9161$$

Where the S_{21} is:

$$S_{21} = 0.0255 - 1.384j = 1.3842\angle -88.9^\circ$$

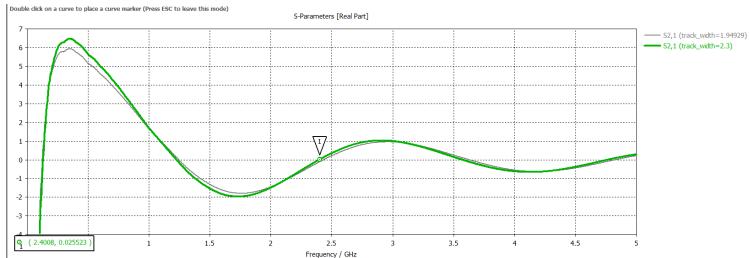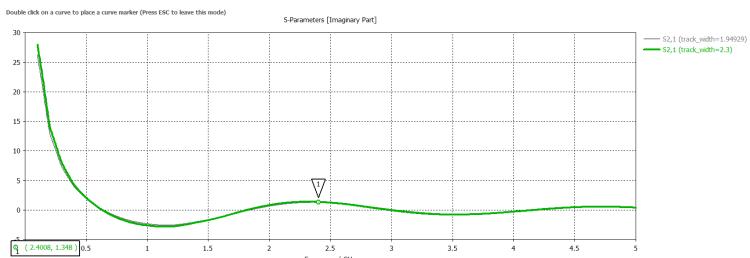Figure 23: Real Part of S_{21} Figure 24: Imaginary Part of S_{21}

2.4.3 Question III

The S-parameters are measured at the connector, as shown in the figure below:

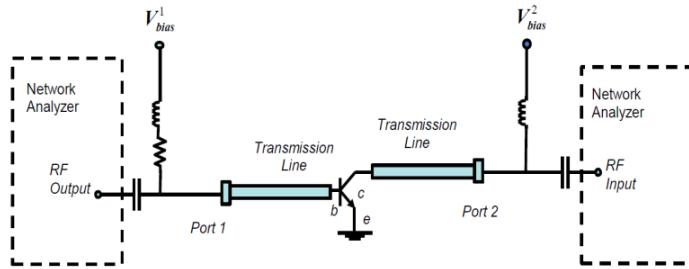


Figure 25: Biasing and decoupling circuit for BJT

the measurement should include the transmission line for simulations, and S-parameter would change due to the transmission line, e.g. Γ_S or Γ_L would rotate in the same VSWR circle, we should take this factor into consideration, as a result, S-parameter should be measured at the connector.

2.5 Task 5

2.5.1 Question I

The parameters are listed below:

$$\begin{aligned} l_{stub,in} &= 21\text{mm} \\ l_{in} &= 25\text{mm} \\ l_{stub,out} &= 7.5\text{mm} \\ l_{out} &= 1\text{mm} \end{aligned}$$

The results are quite different from the calculated values in **Task 2**, then we check the S-parameters in the *s2p* file and at 2.4GHz:

$$S_{11} = 0.929 \angle 129.2^\circ$$

$$S_{21} = 1.442 \angle 41.7^\circ$$

$$S_{12} = 0.042 \angle 29^\circ$$

$$S_{22} = 0.853 \angle 143.3^\circ$$

The S-parameters are different from the given data in task 2, causing different stub and line length, based on this, we can calculate new Γ_S and Γ_L :

$$\Gamma_L = -0.6720 - 0.2284j = 0.71 \angle -161.23^\circ$$

$$Y_L = 0.71 \angle 18.77^\circ$$

$$\Gamma_S = -0.6253 - 0.6353j = 0.8913 \angle -134.54^\circ$$

$$Y_S = 0.8921 \angle 45.46^\circ$$

The stub-matching for the generator can be implemented using the Smith Chart shown below:

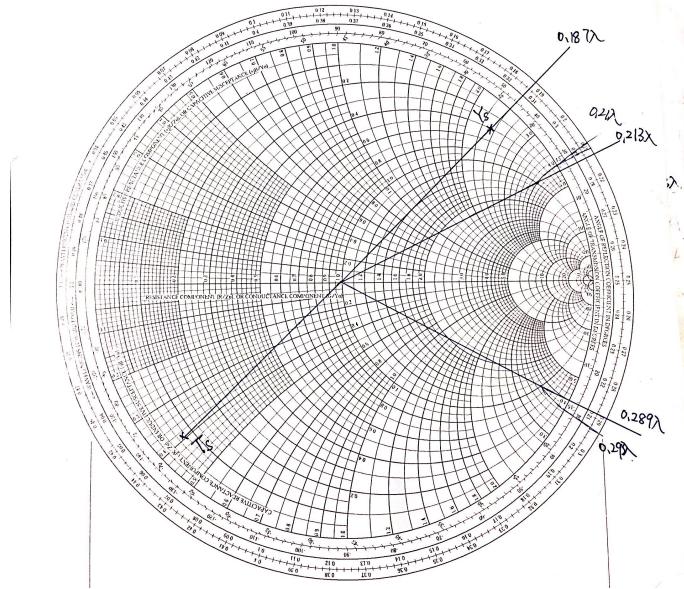


Figure 26: Stub Matching Smith Chart for generator(Γ_S)

Here, from the figure we have two solutions:

$$l_{stub,in1} = 0.21\lambda, l_{in,1} = 0.474\lambda$$

$$l_{stub,in2} = 0.293\lambda, l_{in,2} = 0.398\lambda$$

The stub-matching for the load can be implemented using the Smith Chart shown below:

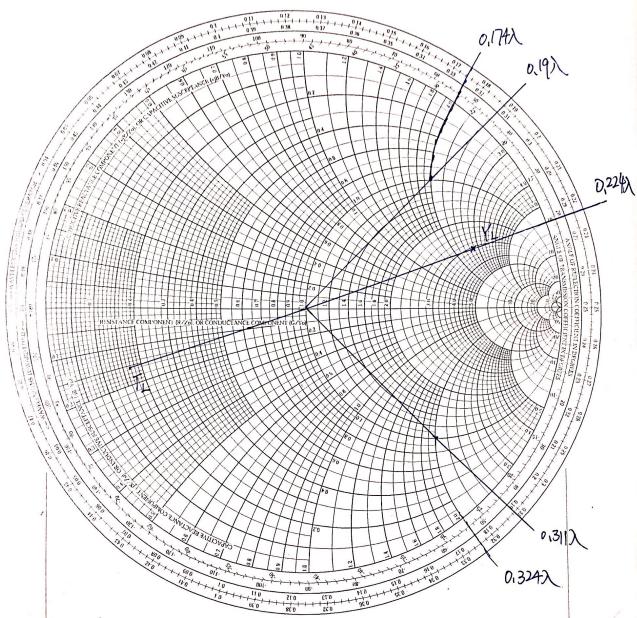


Figure 27: Stub Matching Smith Chart for load(Γ_L)

Also we have two solutions:

$$l_{stub,out1} = 0.174\lambda, l_{out,1} = 0.034\lambda$$

$$l_{stub,out2} = 0.324\lambda, l_{out,2} = 0.413\lambda$$

To conclude:

$$l_{stub,in1} = 0.21\lambda = 14.532mm, l_{in,1} = 0.474\lambda = 32.8mm$$

$$l_{stub,in2} = 0.293\lambda = 20.3mm, l_{in,2} = 0.398\lambda = 27.5416mm$$

$$l_{stub,out1} = 0.174\lambda = 12.04mm, l_{out,1} = 0.034\lambda = 2.353mm$$

$$l_{stub,out2} = 0.324\lambda = 22.42mm, l_{out,2} = 0.413\lambda = 28.58mm$$

The original power gain is about:

$$G_T = 1.9161 = 2.824dB$$

The improved gain should be approximately:

$$G_{T,new} = |S_{21,new}|^2 = \frac{|S_{21}|^2(1 - |\Gamma_L|^2)}{(1 - |\Gamma_S|^2)(|1 - \Gamma_L S_{22}|^2)} = 23.42 = 13.7dB$$

2.5.2 Question II

Based on the stub matching, new S_{11} and S_{22} are:

$$S_{11} = -0.0134 + 0.0735j = 0.0747\angle100.3^\circ$$

$$S_{22} = -0.3541 + 0.2998j = 0.464\angle139.74^\circ$$

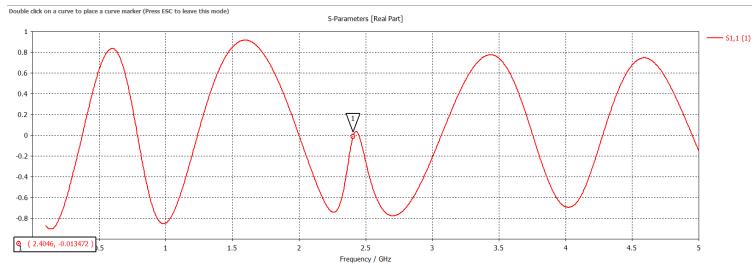


Figure 28: Real Part of S_{11}

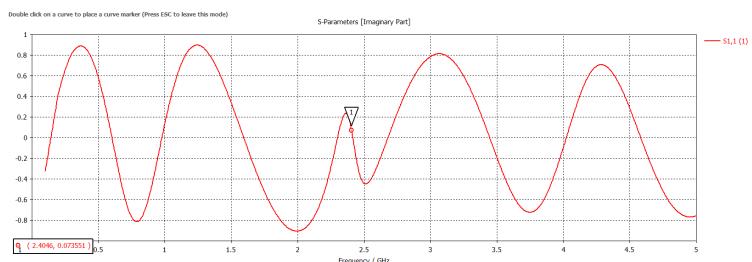
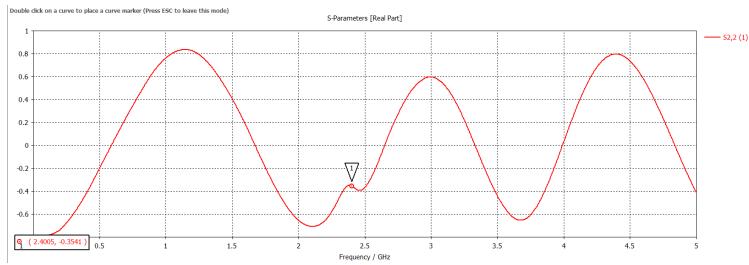
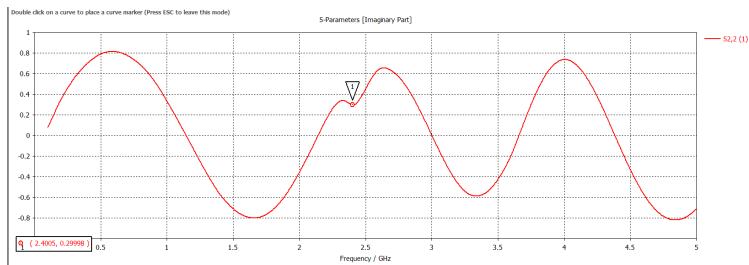


Figure 29: Imaginary Part of S_{11}



Figure 30: Real Part of S_{22} Figure 31: Imaginary Part of S_{22}

2.5.3 Question IIII

The amplifier gain S_{21}^2 is:

$$S_{21} = 2.651 - 0.8j = 2.7691 \angle -16.8^\circ$$

$$G_{max} = |S_{21}|^2 = 7.6679 = 8.9dB$$

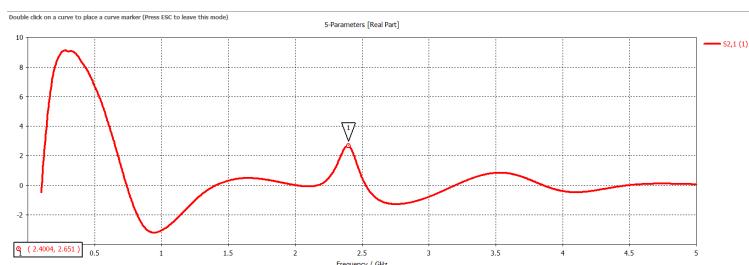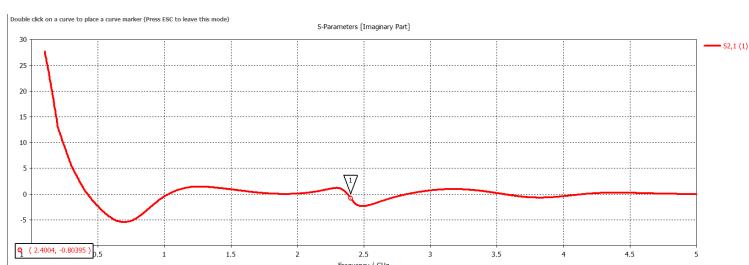Figure 32: Real Part of S_{21} Figure 33: Imaginary Part of S_{21}

The gain is improved but it is not maximised as the input length is not exactly what we calculated, by changing the values to:

$$l_{\text{stub,in}} = 21\text{mm}, l_{\text{in}} = 26\text{mm}$$

$$l_{\text{stub,out}} = 12.04\text{mm}, l_{\text{out}} = 2.353\text{mm}$$

We can reach:

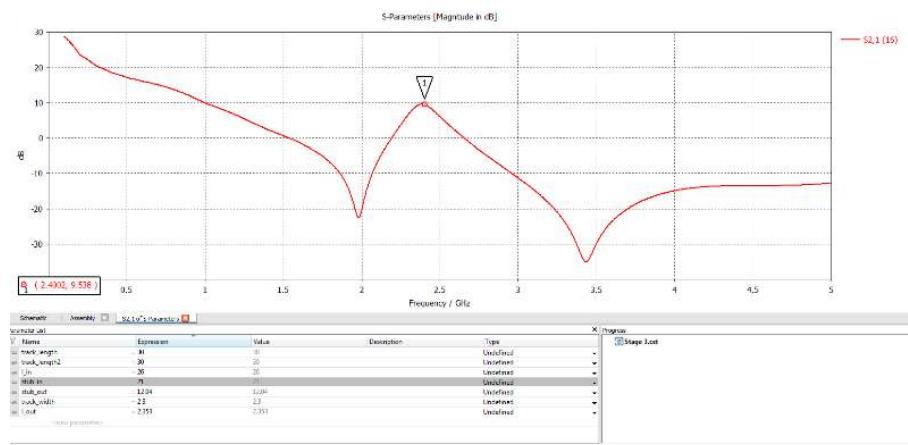


Figure 34: Improved Power Gain S_{21}

S_{21} will improve a little bit to 9.5dB, but still much less than theoretical gain 13.7dB, this is due to the real loss in the transmission line and unmatched impedance as $Z_0 = 49.9\Omega$. Also, the manually measurement of the Smith chart can lead to some error on the input and output length, i.e. $l_{\text{stub,in}}$ and $l_{\text{stub,out}}$ are not matching the maximum gain. The gain can still grow with more precisely values of length. And the approximation of calculation may contribute to the error as well.