



# Engineering Assignment Coversheet

Student Number(s)

813927

855983

753148

Group Code (if applicable):

Please note that you:

- Must keep a full copy of your submission for this assignment
- Must staple this assignment
- Must NOT use binders or plastic folders except for large assignments

<b>Assignment Title:</b>	Voltage Controlled Oscillator and Cascode Amplifier
<b>Subject Number:</b>	ELEN90062
<b>Subject Name:</b>	High Speed Electronics
<b>Student Name:</b>	Rui Yuan, Huawang Liu, Haotian Xia
<b>Lecturer/Tutor:</b>	
<b>Due Date:</b>	28/08/2018

## For Late Assignments Only

Has an extension been granted? Yes / No (circle)

A per-day late penalty may apply if you submit this assignment after the due date/extension. Please check with your Department/coordinator for further information.

## Plagiarism

Plagiarism is the act of representing as one's own original work the creative works of another, without appropriate acknowledgment of the author or source.

## Collusion

Collusion is the presentation by a student of an assignment as his or her own which is in fact the result in whole or in part of unauthorised collaboration with another person or persons. Collusion involves the cooperation of two or more students in plagiarism or other forms of academic misconduct.

Both collusion and plagiarism can occur in group work. For examples of plagiarism, collusion and academic misconduct in group work please see the University's policy on Academic Honesty and Plagiarism:

<http://academichonesty.unimelb.edu.au/>

Plagiarism and collusion constitute cheating. Disciplinary action will be taken against students who engage in plagiarism and collusion as outlined in University policy. Proven involvement in plagiarism or collusion may be recorded on my academic file in accordance with Statute 13.1.18.

## STUDENT DECLARATION

Please sign below to indicate that you understand the following statements:

I declare that:

- This assignment is my own original work, except where I have appropriately cited the original source.
- This assignment has not previously been submitted for assessment in this or any other subject.

For the purposes of assessment, I give the assessor of this assignment the permission to:

- Reproduce this assignment and provide a copy to another member of staff; and
- Take steps to authenticate the assignment, including communicating a copy of this assignment to a checking service (which may retain a copy of the assignment on its database for future plagiarism checking).

Student signature

*Haotian Xia*  
*Rui Yuan Huawang*

Date 28/08/2018



University of Melbourne  
ELEN90062 High Speed Electronics  
WORKSHOP

# WORKSHOP 2 REPORT

---

Rui YUAN  
813927  
Huawang Liu  
855983  
Haotian Xia  
753148

August 28, 2018

---

# I Colpitts Oscillator Simulation

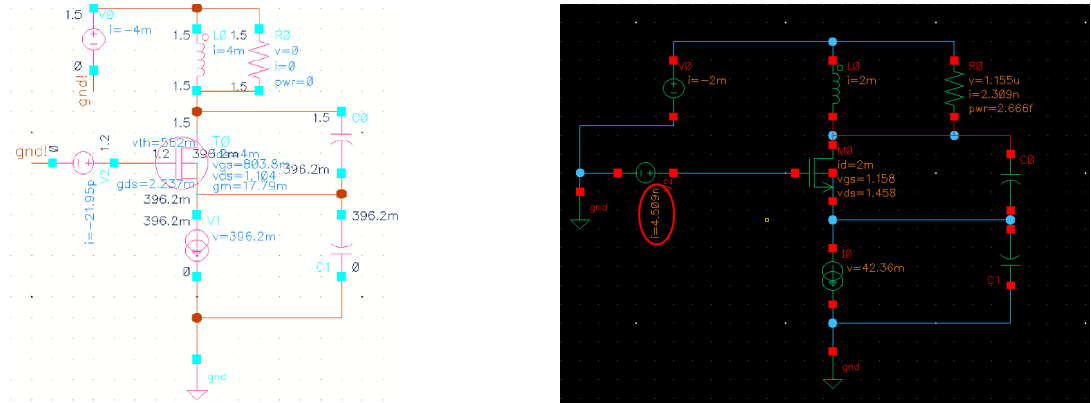


Figure 1: Given and built Colpitts Oscillator Circuit

## I.1 Exclusive Summary

In the first circuit, we consider important design issues of the oscillator (frequency, amplitude, and condition of start up). We then complement the Colpitts Oscillator circuit as above, and compare its simulation performance with theoretical values. We find the exist difference may caused by parasitic capacitors.

## I.2 Calculate the minimum gain ( $g_m$ ), required to start the oscillations.

As we are given  $L = 1nH$ ,  $C1 = C2 = 24pF$ , and  $R = 500\Omega$  respectively, at resonance when transconductance is minimum to guarantee startup:

$$\frac{ng_m R}{n^2 g_m R + 1} = 1 \quad (1)$$

Yields, we need

$$g_m > \frac{1}{R(n - n^2)} \quad (2)$$

Where the capacitor ratio  $n$  is:

$$\begin{aligned} n &= \frac{C1}{C1 + C2} \\ &= \frac{1}{2} \end{aligned} \quad (3)$$

Hence:

$$\begin{aligned} g_m &> \frac{1}{500 \times \left(\frac{1}{4}\right)} \\ &> 8mS \end{aligned} \quad (4)$$

Which means the minimum necessary  $g_m$  to start oscillation is  $8mS$ .

### I.3 Calculate the frequency of oscillations, $f$ .

$$\begin{aligned} f &= \frac{1}{2\pi\sqrt{L\left(\frac{C_1C_2}{C_1+C_2}\right)}} \\ &= \frac{1}{2\pi\sqrt{1 \times 10^{-9} \frac{(24 \times 10^{-12})^2}{48 \times 10^{-12}}}} \\ &\approx 1.453 \times 10^9 = 1.453GHz \end{aligned} \quad (5)$$

### I.4 Implement the circuit

From figure 1, we choose nmos24 NMOS transistor model. To get a unit loop transmission magnitude, **we need to balance the source current and drain current** as the figures below. When comparing the different widths of NMOS, we can obtain the balanced point between MOS and current. After several trials, the width of NMOS is obtained.

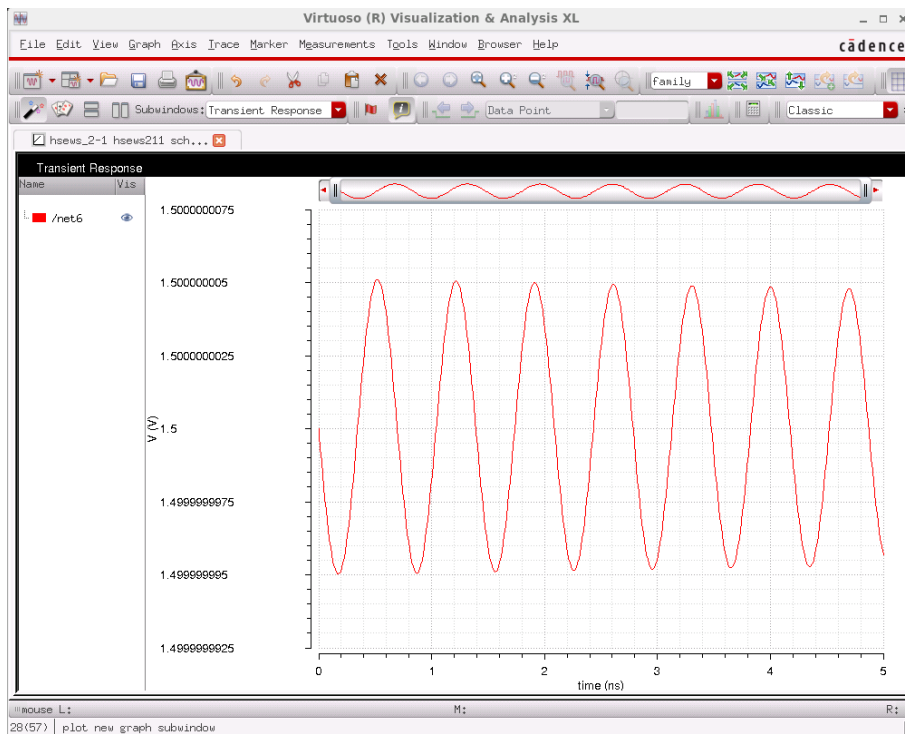


Figure 2: 400um width of NMOS

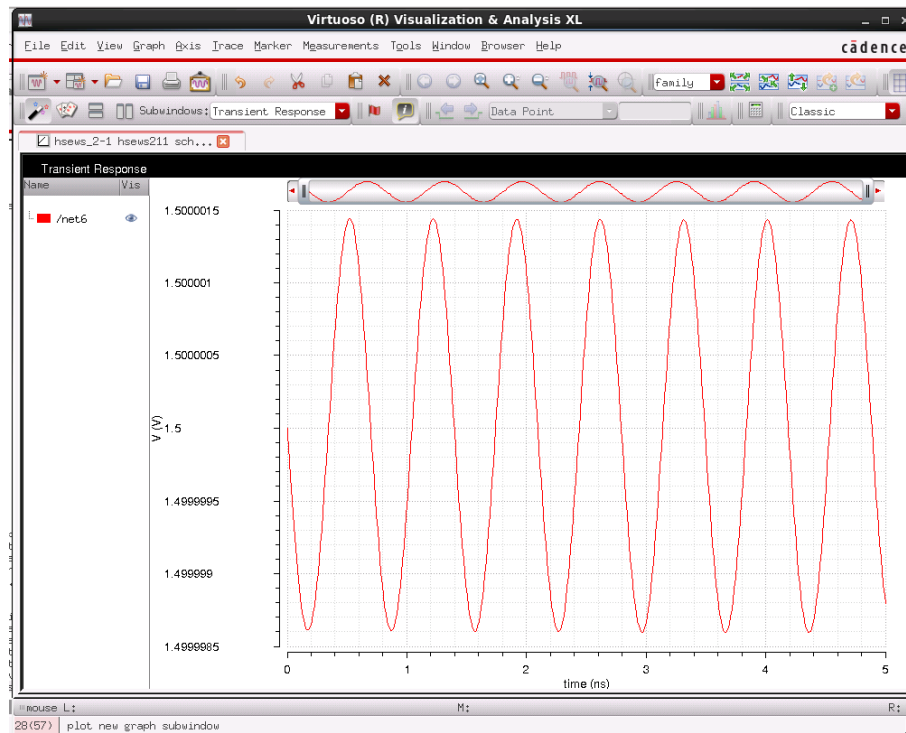


Figure 3: 570um width of NMOS

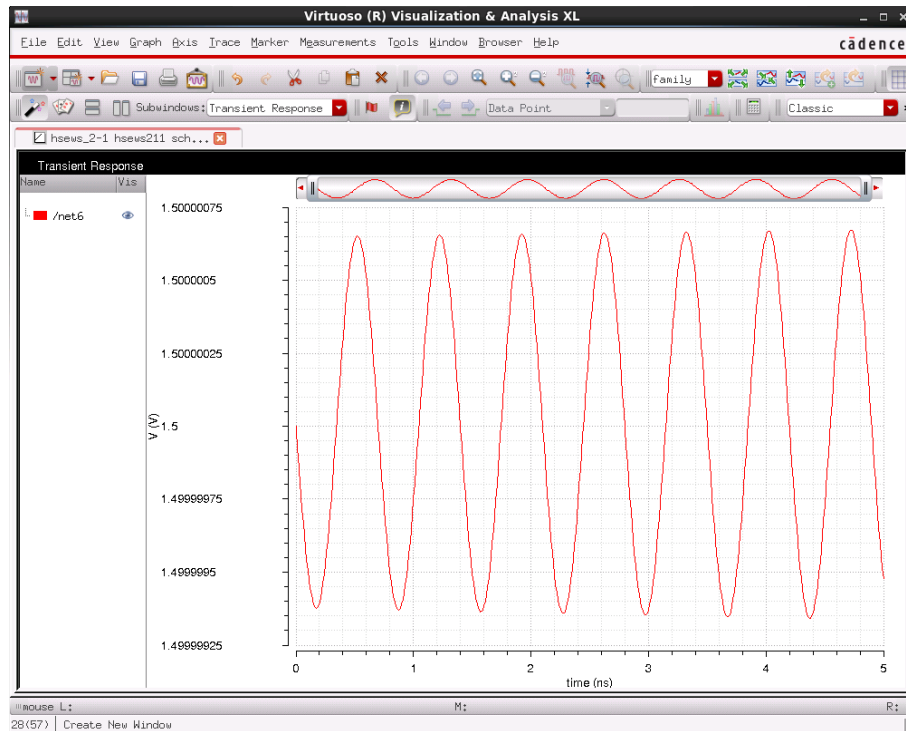


Figure 4: 700um width of NMOS

Hence, we set the 570um width NMOS transistor and the the 2mA current source.

## I.5 set maxstep and observe the output signal

To get more than 10 simples period period of the signal, we need:

$$\begin{aligned} maxstep &< \frac{0.1}{f} \\ &< 66.7ps \end{aligned} \quad (6)$$

Yielding, we set maximum step to  $10ps$ . it is also shown in figure 5:



Figure 5: parameter set for maximum step

## I.6 Simulation and calculation compare

From figure below, we find a significant difference between simulated and calculated values of frequency. which is  $f = \frac{1}{697.911} \times 10^{12} = 1.43GHz$ , the real frequency is  $20MHz$  less than the calculation result. **The main reason is because the parasitic capacitors in the transistor which do not be considered in our calculations.** From the perspective of amplitude, since the bias current is  $4.5nA$  in figure 1,  $V_{tank} = 2I_{bias}R(1 - n) = 2.25uV$

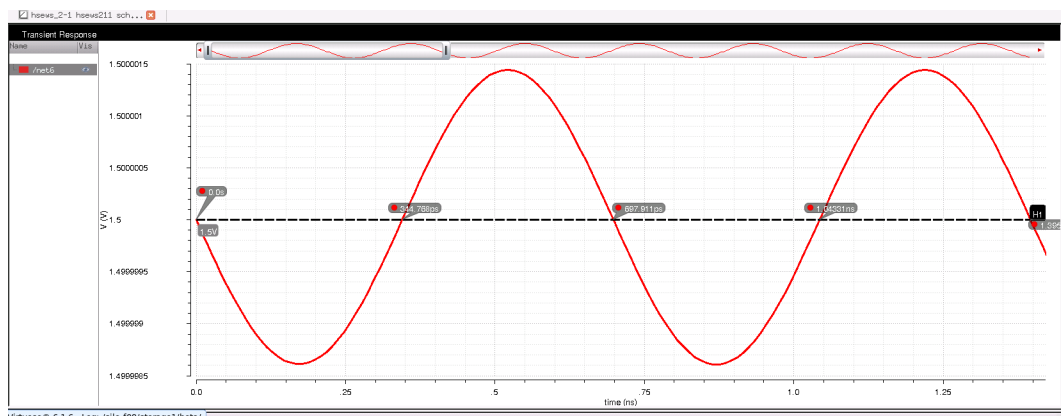


Figure 6: Real frequency plot

## II Input Matching of Cascode Amplifier at 1.5 GHz

### II.1 Executive Summary

In this part, the circuit is a cascode amplifier, the resistant is not match at the input of the signal by measuring the load resistance. the matching based on L-matching circuit is designed in this part, by doing the simulation and calculation, the final result is obtained and the value of serial inductor is  $7.8312nH$  and the parallel capacitor is  $7.294pF$

### II.2 Build the circuit and bias the transistor

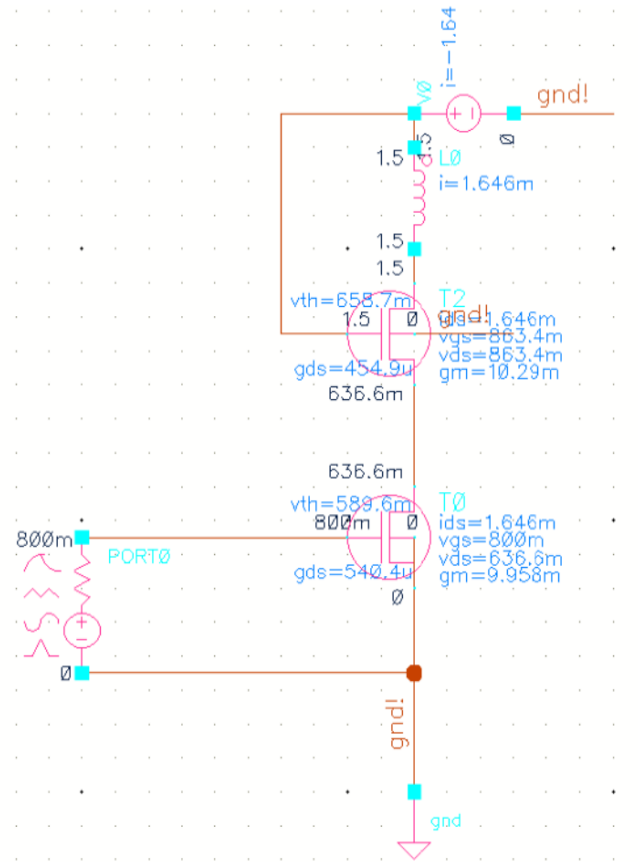


Figure 7: Cascode Amplifier Circuit

### II.3 Simulate S-Parameter of the input port

The plotted S-Parameter is as below:

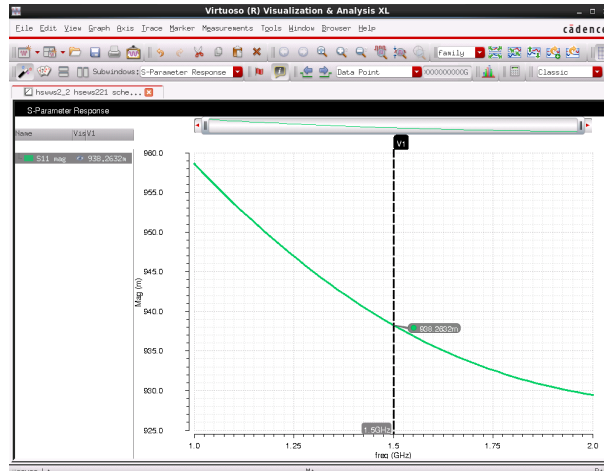


Figure 8: non-matching S parameter

From the figure 8, we can state almost all power is reflected. Under this condition, we need to match our source impedance and load impedance.

## II.4 Design an input L-matching circuit

Firstly, we plotted  $Z_l$  to find the load impedance at  $1.5\text{GHz}$  is as below, we have  $R_l = 3.902\omega$  and  $X_l = 60.1428\Omega$ :

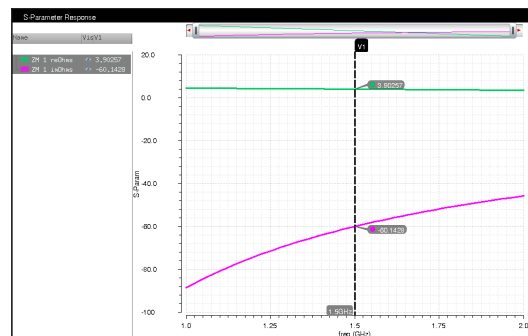


Figure 9: The measured load impedance at Port Zero

By comparing the resistance of  $R_S$  and  $R_L$ , we should boost our input impedance. Yields, we connect the load in series with the inductance and build the L-match circuit as below:



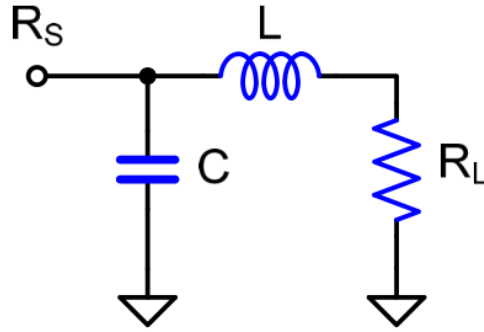


Figure 10: Implemented L-match circuit

From the L-matching circuit we build, and follow the L-matching procedure in lecture four:

$$R_{hi} = \max(R_S, R_L) = 50\Omega \quad (7)$$

$$R_{lo} = \min(R_S, R_L) = 3.902\Omega \quad (8)$$

$$m = \frac{R_{hi}}{R_{lo}} = 12.812 \quad (9)$$

$$Q = \sqrt{m - 1} = 3.437 \quad (10)$$

$$X_s = Q \cdot R_L = 13.412 \quad (11)$$

$$X_p = -X_s \cdot (1 + Q^{-2}) = -14.548 \quad (12)$$

$$C = -1/(X_p \times 2\pi \times f) = 7.294\text{pf} \quad (13)$$

$$H = (X_s - X_l)/(2\pi \times f) = 7.8312\text{nH} \quad (14)$$

the designed L matching circuit in the cadence is shown in Figure 11

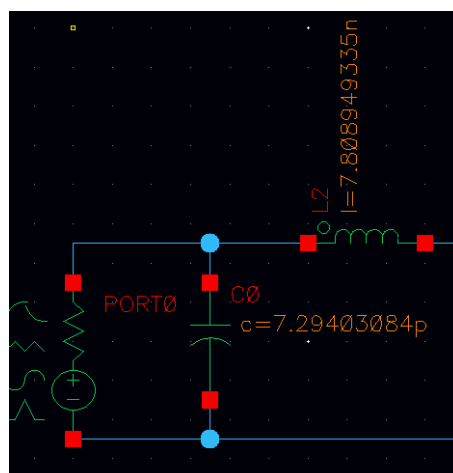


Figure 11: matching circuit

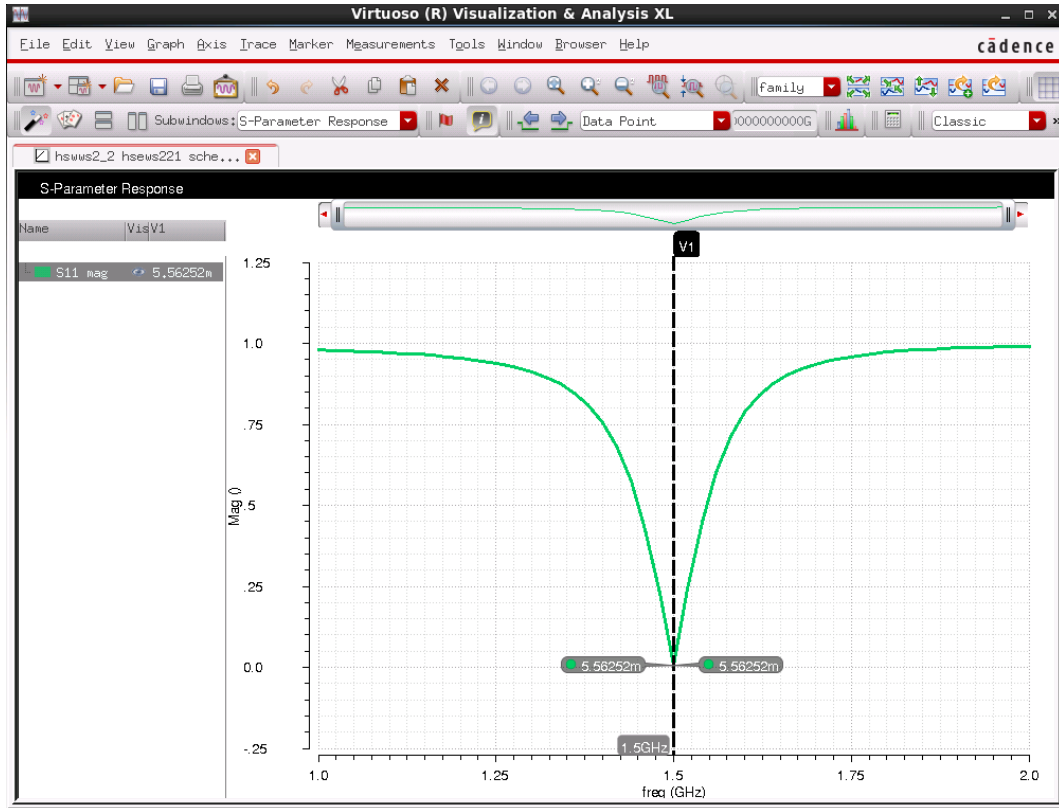


Figure 12: S parameter after matching circuit

After implementing our L-matching circuit, we regenerate S-Parameter in figure 12. **The new S-Parameter we get at 1.5GHz is 0.005.** We can state the reflection coefficient is almost zero at required frequency which means our circuit is nearly perfect match at the selected frequency. **The reason why the S-Parameter is not exact zero at 1.5GHz is because our accuracy limit on those components parameters.** If we want to increase the selectivity of our circuit, a possible solution is use a  $\pi$  match circuit which can provide flexibility on Q value. We can also state the same conclusion by the smith chart as below:

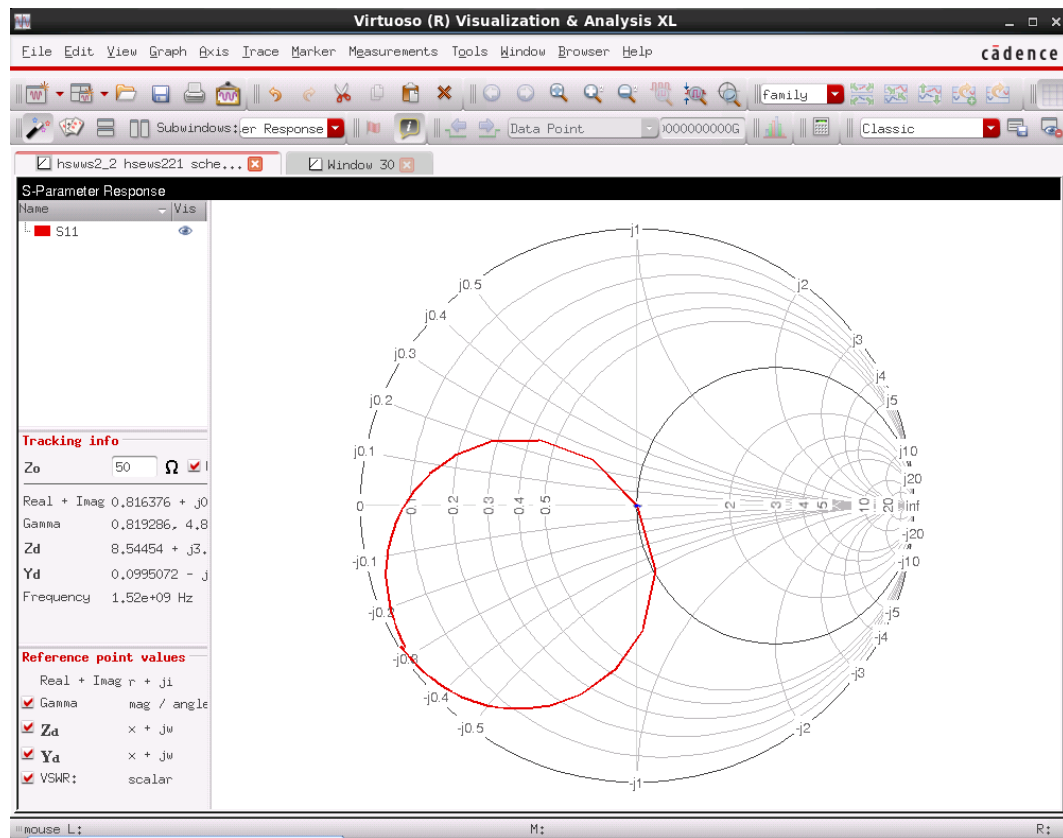


Figure 13: smith plot after matching